

DETERMINATION OF ERRORS
IN A
SERIES TRANSFORMER

BY

E. M. BEATY and V. F. VACEK

Armour Institute of Technology

1908

537.838

B 38



Illinois Institute
of Technology
UNIVERSITY LIBRARIES

AT 103

Beatty, E. M.

Determination of errors in a
series transformer

For Use In Library Only

DETERMINATION OF ERRORS
IN A
SERIES TRANSFORMER

A THESIS

PRESENTED BY

E. M. BEATY

V. F. VACEK

TO THE

PRESIDENT AND FACULTY

OF

ARMOUR INSTITUTE OF TECHNOLOGY

FOR THE DEGREE OF

BACHELOR OF SCIENCE IN ELECTRICAL ENGINEERING

HAVING COMPLETED THE PRESCRIBED COURSE OF STUDY IN

ELECTRICAL ENGINEERING

JUNE 1908

ILLINOIS INSTITUTE OF TECHNOLOGY
PAUL V. GALVIN LIBRARY
35 WEST 33RD STREET
CHICAGO IL 60616

Approved

Albert S. Rutledge

Prof. of Elec. Eng.

H. M. Nagel

Dean of Engineering

L. C. Moore
Chairman of Committee

It was intended at the outset to run a test on several transformers of various types, but it was later found that the subject took a great deal more time than was anticipated. For this reason a full set of data was obtained on only one transformer.

The calculated data and the curves shown in this thesis are those for a General Electric Series Transformer, Type S, Form D, #50286, built for 13500 volts on the mains. Ratio 20 to 1. Full load 75 amperes, thirty minute load 100 amperes.

Further data on a 25 ampere transformer is included in this thesis but it is not worked up.

A series transformer is a device commonly used in high potential power lines for supplying current to an ammeter or the series coil of a wattmeter.

It being undesirable to bring the high potential feeders directly to the switch board on account of the danger thus involved the series transformer was developed.

It occupies the same place in alternating current work as does the shunt in direct current lines, namely; that of supplying a definite ratio of the total current flowing through the lines to instruments whose scales are so calibrated that the total amount of current flowing is read, instead, of just that portion which flows through them.

The transformer is essentially a few turns of heavy wire, wound on a porcelain core, which ^{are} connected in series with the line, in which the current is to be measured. The secondary consists of a large number of smaller turns wound around the primary winding. The measuring instruments connect directly to these secondary terminals.

If the transformer is designed for some particular instrument with its known length of leads from the transformer to the switch board it can be so constructed that the percent error on all loads is very small.

As the above is very seldom the case, since certain types of transformers are used on different types of instruments and different lengths of leads, an error is introduced which depends upon the nature of the secondary circuit and the size of the load.

The commonly recognized error of these transformers is that of variation of the ratio of transformation. Another source of

error, which is seldom mentioned is that of the phase relations of the currents in the primary and secondary of the transformer. The error caused by this latter is practically negligible at unity power factor but rapidly increases for lower power factors.

In a transformer the primary and secondary currents are nearly always assumed to be 180° apart. This is very seldom the case but does not make much difference in general cases.

In a series transformer where its sole function is to supply current for power measuring instruments an error, however small, causes a loss where large amounts of power are measured.

The current in the secondary of a transformer of the series type instead of being just 180° behind the current in the primary, ^(the 180° position) lags it by a small angle which will be called alpha (α) in this work.

The object of the following work is to find the value of that angle and also the ratio of transformation under different characters of secondary circuits for loads varying from light loads to over loads. The value of the ratio of transformation is a very easy quantity to obtain since it is just the ratio of the primary to the secondary current and these values can be obtained very ~~rapidly~~ ^{readily}. The method of obtaining the phase angle was a harder matter as the literature on that subject was of very meagre nature. The only reference found, was that in the transactions of the American Institute of Electrical Engineers of 1906.

An oscillograph was thought of, but as the angle to be measured ~~is~~ ^{was} so small compared to the scale of the oscillograms which could be obtained, that another method was thought more applicable.

The method used is a rather simple one and consists of two sensitive dynamometers, the stationary coils of which are connected in parallel, one of them first going through an ammeter.

3

These coils are then connected through a bank of lamps to the secondary of a three phase, squirrel cage, induction motor, the secondaries of each phase being open and connected to sliprings. By supplying current to the primary of the induction motor a revolving field is set up and by moving the rotor the desired amount and clamping it in place, a current which varies from the primary current by an amount equal to from zero to 120° depending upon the position of rotor, can be obtained.

The moving coil of one dynamometer was connected to a shunt in the primary circuit. The moving coil of the other dynamometer was connected through an ammeter to the secondary of the transformer to be tested. A double pole switch was placed in each circuit so that the instruments could be cut out when desired. A single pole switch was placed across the secondary terminals of the transformer so it could be shorted when the other switches were open. This was necessary because if it was left open a high e.m.f. would be set up in the secondary due to the primary current. This e.m.f. would be liable to puncture the insulation.

As a large current was needed the most convenient way of obtaining it was decided to be that, of using a high current transformer, which had a ratio of eleven, twenty-two, forty-four, depending upon the way of connecting. A current as high as three thousand amperes could be obtained with this if desired but as only one hundred was needed it was connected up with the twenty-two ratio and by varying^y the current in the primary by means of a lamp rack and some carbon rheostats the value of the secondary current of this transformer could be changed at will.

4

The secondary of this transformer was connected directly through the primary of the series transformer and the shunt spoken of before.

A frequency meter was also supplied, as were double-throw switches for balancing the dynamometers against each other if desired. The scheme of wiring can easily be seen from the accompanying blue print.

The method of working the apparatus is as follows: Current is sent through both coils of the dynamometer by manipulation of the lamp racks. Then by moving the handle connected to the rotor of the induction motor the phase relation of the current in the stationary coils is adjusted to 90° difference from that in the moving coil of the dynamometer connected onto the shunt. The current in the coil connected to the shunt is in phase with the primary current of the transformer. A 90° difference in phase relation of the currents will cause the dynamometer connected to the shunt to read zero.

If the current in the secondary of the transformer is just 180° out of phase with the primary current the dynamometer across it will read zero. If it does not read zero, the deflection is noted and the values of the currents in each of its coils are taken. The deflection obtained is proportional to the sine of the angle of lag since the deflection of the dynamometer is equal to the products of the currents through each coil times the cosine of the angle between them or $D = K I_1 I_2 \cos \theta$. By adjusting the dynamometer across the shunt for zero deflection θ becomes 90° so the angle between the currents in the second dynamometer is $(90^\circ - a)$. Therefore $D = K I_1 I_2 \cos(90^\circ - a) = K I_1 I_2 \sin(a)$.

The dynamometer was calibrated as an ammeter on direct current so the value of the cosine ^{was} ~~is~~ one and as the two coils were in series $I_1 = I_2$, then $D = KI_1^2$. This enabled one to determine the value of K for different deflections and a curve was plotted so these values could be taken off. The ammeters were calibrated and curves plotted for them as was also done for all the instruments used.

When the experiment first started an ammeter was placed in the circuit of the moving coil connected across the shunt so by ratio of the resistance of these two circuits and the reading of the ammeter in the secondary of the transformer the ratio of transformation could be obtained directly. This cut down the sensibility of the dynamometer so much that it was taken out and the ratio obtained separately by means of a hot wire ammeter connected across the shunt. By plotting a curve for these ratio readings the value of the primary current corresponding to the secondary current taken during the phase angle readings could be obtained and the ratio obtained by their division.

In order to obtain the impedance of the secondary circuit a special instrument had to be used because there was no low reading alternating current voltmeter obtainable. In order to obtain an instrument, a Whitney hot wire ammeter which is commonly used across a shunt was calibrated as a voltmeter as follows:

It was placed across the shunt and readings taken of current flowing through the shunt and the reading of ammeter. A milli-voltmeter was then placed across the shunt and readings of it taken corresponding to line current. By plotting a curve against ammeter readings and milli-volt readings the calibration of the ammeter as a voltmeter was obtained.

In obtaining the impedance drops, the drop had to be taken over the ammeter which was in the circuit or the true value of current flowing through the circuit could not be obtained. As this could not always be done it was necessary to calibrate the instrument as an ammeter without its shunt. Then by subtracting the current flowing through it from the ammeter reading the true value of the current in the circuit was obtained and then $Z = \frac{E}{I}$ where E is the voltage as indicated by the instrument and I is the corrected current. This was necessary because the instrument had such a low resistance that more current flowed through it, than did through the circuit to be measured. The resistance of the circuit was obtained by the fall of potential method using a calibrated ammeter and voltmeter.

7

The symbols and letters used in this work have the following meanings:

- R_s : Resistance of secondary circuit.
 L : Reactance of secondary circuit.
 I_{ph} : Current in phase-shifter.
 I_s : Current in transformer secondary.
 I_p : Current in transformer primary.
Defl. : Dynamometer deflection.
 K : Dynamometer constant.
 R : Ratio of primary current to secondary current.
 $\#$: Corrected values of above symbols.

The circuits used are composed of the following; as taken from the data sheets on resistance and impedance.

| No. | Character. |
|-----|------------|
| 1 | (a) |
| 3 | (b) + (c) |
| 4 | (a) + (c) |
| 5 | (c) + (h) |
| 6 | (c) + (i) |
| 7 | (e) |
| 8 | (f) |
| 10 | (g) |
| 11 | (k) + (c) |

The nature of the secondary circuits used are as follows:

| No. | R | L |
|-----|--------|----------|
| 4 | .35460 | .0035860 |
| 5 | " | .0058000 |
| 11 | " | .0096260 |
| 13 | " | .0166000 |
| 6 | " | .0228000 |
| 1 | .09060 | .0003460 |
| 7 | .12870 | " |
| 12 | .21200 | " |
| 8 | .22920 | " |
| 10 | .25900 | " |
| 3 | .32060 | .0010740 |

(a) Resistance. (b)

| I | E | #I | #E | R | I | E | #I | #E | R |
|---|-------|------|-------|-------|---|-------|------|-------|--------|
| 1 | 0.270 | 0.99 | 0.260 | 0.263 | 1 | 0.135 | 0.99 | 0.130 | 0.1315 |
| 2 | 0.530 | 1.98 | 0.520 | 0.263 | 2 | 0.265 | 1.98 | 0.265 | 0.1337 |
| 3 | 0.795 | 2.96 | 0.790 | 0.267 | 3 | 0.392 | 2.96 | 0.380 | 0.1283 |
| 4 | 1.050 | 3.89 | 1.035 | 0.266 | 4 | 0.520 | 3.89 | 0.510 | 0.1278 |
| 5 | 1.300 | 4.86 | 1.270 | 0.262 | 5 | 0.640 | 4.86 | 0.625 | 0.1286 |

| (c) | | | | | (d) | | | | |
|-----|-------|------|-------|--------|-----|-------|------|-------|--------|
| I | E | #I | #E | R | I | E | #I | #E | R |
| 1 | 0.090 | 0.99 | 0.090 | 0.0910 | 1 | 0.105 | 0.99 | 0.105 | 0.1062 |
| 2 | 0.180 | 1.98 | 0.175 | 0.0885 | 2 | 0.210 | 1.98 | 0.205 | 0.1035 |
| 3 | 0.275 | 2.96 | 0.270 | 0.0913 | 3 | 0.230 | 2.96 | 0.310 | 0.1047 |
| 4 | 0.368 | 3.89 | 0.360 | 0.0903 | 4 | 0.425 | 3.89 | 0.415 | 0.1040 |
| 5 | 0.455 | 4.86 | 0.445 | 0.0917 | 5 | 0.525 | 4.86 | 0.510 | 0.1050 |

| (e) | | | | | (f) | | | | |
|-----|-------|------|-------|--------|-----|-------|------|-------|--------|
| I | E | #I | #E | R | I | E | #I | #E | R |
| 1 | 0.238 | 0.99 | 0.237 | 0.2495 | 1 | 0.132 | 0.99 | 0.130 | 0.1315 |
| 2 | 0.465 | 1.98 | 0.455 | 0.2300 | 2 | 0.258 | 1.98 | 0.250 | 0.1265 |
| 3 | 0.690 | 2.96 | 0.670 | 0.2265 | 3 | 0.392 | 2.96 | 0.380 | 0.1285 |
| 4 | 0.920 | 3.89 | 0.900 | 0.2310 | 4 | 0.513 | 3.89 | 0.500 | 0.1265 |
| 5 | 1.135 | 4.86 | 1.100 | 0.2290 | 5 | 0.640 | 4.86 | 0.625 | 0.1285 |

| (g) | | | | |
|-----|-------|------|------|-------|
| I | E | #I | #E | R |
| 1 | 0.262 | 0.99 | 0.26 | 0.263 |
| 2 | 0.520 | 1.98 | 0.51 | 0.257 |
| 3 | 0.775 | 2.96 | 0.76 | 0.257 |
| 4 | 1.035 | 3.89 | 1.01 | 0.260 |
| 5 | 1.283 | 4.86 | 1.25 | 0.257 |

11
12
13
14
15

16
17
18
19
20

21
22
23
24
25

26
27
28
29
30

31
32
33
34
35

36
37
38
39
40

41
42
43
44
45

Impedance.

(a)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|-------|
| 1.423 | 40.0 | 50/50 | 1.430 | 1.245 | 0.185 | 0.117 | 0.633 |
| 2.132 | 60.0 | " | 2.165 | 1.860 | 0.305 | 0.171 | 0.562 |
| 2.808 | 80.0 | " | 2.830 | 2.440 | 0.390 | 0.229 | 0.588 |
| 3.150 | 90.0 | " | 3.185 | 2.730 | 0.455 | 0.257 | 0.565 |
| 3.478 | 100.0 | " | 3.525 | 3.000 | 0.525 | 0.286 | 0.545 |

(b)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|--------|
| 1.890 | 40.0 | 50.50 | 1.915 | 1.245 | 0.670 | 0.117 | 0.1750 |
| 2.800 | 60.0 | " " | 2.825 | 1.860 | 0.965 | 0.171 | 0.1775 |
| 3.738 | 80.0 | " | 3.785 | 2.440 | 1.345 | 0.229 | 0.1700 |
| 4.600 | 100.0 | " | 4.65 | 3.000 | 1.650 | 0.286 | 0.1735 |

(c)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|--------|
| 0.550 | 20.0 | 50.50 | 0.530 | 0 | 0.530 | 0.064 | 0.121 |
| 1.085 | 40.0 | " | 1.085 | 0 | 1.085 | 0.117 | 0.108 |
| 1.600 | 60.0 | " | 1.600 | 0 | 1.600 | 0.171 | 0.107 |
| 2.148 | 80.0 | " | 2.165 | 0 | 2.165 | 0.229 | 0.106 |
| 2.375 | 90.0 | " | 2.405 | 0 | 2.405 | 0.257 | 0.1068 |
| 2.650 | 100.0 | " | 2.675 | 0 | 2.675 | 0.286 | 0.107 |
| 1.075 | 40.0 | 51.60 | 1.075 | 0 | 1.075 | 0.117 | 0.1088 |
| 1.600 | 60.0 | " | 1.610 | 0 | 1.610 | 0.171 | 0.106 |
| 2.185 | 80.0 | " | 2.225 | 0 | 2.225 | 0.229 | 0.103 |
| 2.435 | 90.0 | " | 2.470 | 0 | 2.470 | 0.257 | 0.104 |
| 2.718 | 100.0 | " | 2.750 | 0 | 2.750 | 0.286 | 0.104 |

Impedance.

(d)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|------|---------|-----------|-------|-------|--------|
| 0.875 | 40.0 | 51.0 | 0.875 | 0 | 0.875 | 0.117 | 0.1340 |
| 1.335 | 60.0 | " | 1.339 | 0 | 1.339 | 0.171 | 0.1275 |
| 1.818 | 80.0 | " | 1.835 | 0 | 1.835 | 0.229 | 0.1250 |
| 2.028 | 90.0 | " | 2.040 | 0 | 2.040 | 0.257 | 0.1400 |
| 2.26 | 100.0 | " | 2.290 | 0 | 2.290 | 0.286 | 0.1250 |

(h)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|-------|
| 1.345 | 40.0 | 50.50 | 1.345 | 1.245 | 0.100 | 0.117 | 1.170 |
| 1.960 | 60.0 | " | 1.980 | 1.860 | 0.120 | 0.171 | 1.425 |
| 2.550 | 80.0 | " | 2.556 | 2.440 | 0.110 | 0.229 | 2.80 |
| 3.165 | 100.0 | " | 3.200 | 3.000 | 0.200 | 0.286 | 1.430 |

(i)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|------|
| 0.790 | 24.0 | 50.25 | 0.780 | 0.760 | 0.02 | 0.076 | 3.80 |
| 1.275 | 40.0 | " | 1.275 | 1.245 | 0.030 | 0.117 | 3.90 |
| 1.870 | 60.0 | " | 1.900 | 1.860 | 0.04 | 0.171 | 4.50 |
| 2.445 | 80.0 | " | 2.460 | 2.440 | 0.020 | 0.229 | 1.44 |
| 3.030 | 100.0 | " | 3.060 | 3.000 | 0.060 | 0.286 | 4.75 |

(k)

| I_2 | E_H | Alt. | # I_2 | $I_{H.W}$ | I_c | E | Z |
|-------|-------|-------|---------|-----------|-------|-------|-------|
| 1.380 | 40.0 | 50.50 | 1.370 | 1.245 | 0.115 | 0.117 | 1.017 |
| 2.050 | 60.0 | " | 2.060 | 1.860 | 0.200 | 0.171 | 0.850 |
| 2.695 | 80.0 | " | 2.710 | 2.440 | 0.270 | 0.229 | 0.850 |
| 3.310 | 100.0 | " | 3.350 | 3.000 | 0.350 | 0.286 | 0.820 |

Ratio Readings.

| I_H | I_L | I_P | I_S | I_H | I_L | I_P | I_S |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 8.0 | 0.50 | 11.5 | 0.50 | 12.0 | 0.60 | 15.5 | 0.60 |
| 19.9 | 1.13 | 22.8 | 1.13 | 22.0 | 1.21 | 24.5 | 1.21 |
| 31.0 | 1.63 | 32.5 | 1.65 | 32.0 | 1.62 | 33.5 | 1.64 |
| 40.0 | 2.08 | 41.0 | 2.10 | 40.0 | 2.08 | 41.0 | 2.10 |
| 50.0 | 2.56 | 51.0 | 2.56 | 50.0 | 2.55 | 51.0 | 2.55 |
| 60.0 | 3.07 | 61.2 | 3.11 | 60.0 | 3.09 | 61.2 | 3.13 |
| 70.0 | 3.63 | 71.8 | 3.68 | 70.0 | 3.68 | 71.8 | 3.73 |
| 80.0 | 4.10 | 82.0 | 4.15 | 80.0 | 4.14 | 82.0 | 4.20 |
| 90.0 | 4.60 | 91.3 | 4.65 | 90.0 | 4.65 | 91.3 | 4.70 |
| 96.8 | 4.98 | 97.8 | 4.98 | 95.2 | 4.97 | 96.5 | 4.98 |

Circuit #4

| I_H | I_L | I_P | I_S |
|-------|-------|-------|-------|
| 10.0 | 0.58 | 13.5 | 0.58 |
| 22.0 | 1.20 | 24.5 | 1.21 |
| 30.0 | 1.55 | 31.7 | 1.56 |
| 40.0 | 2.08 | 41.0 | 2.09 |
| 50.0 | 2.55 | 51.0 | 2.61 |
| 60.0 | 3.09 | 61.2 | 3.13 |
| 70.0 | 3.65 | 71.8 | 3.70 |
| 80.0 | 4.11 | 82.0 | 4.16 |
| 90.0 | 4.63 | 91.3 | 4.68 |
| 95.0 | 4.95 | 96.2 | 4.97 |

4
 5
 6
 7
 8
 9
 10
 11
 12
 13
 14
 15

一
 二
 三
 四
 五
 六
 七
 八
 九
 十

8
 9
 10
 11
 12
 13
 14
 15

100

一、二、三、四、五、六、七、八、九、十、十一、十二、十三、十四、十五、十六、十七、十八、十九、二十、二十一、二十二、二十三、二十四、二十五、二十六、二十七、二十八、二十九、三十、三十一、三十二、三十三、三十四、三十五、三十六、三十七、三十八、三十九、四十、四十一、四十二、四十三、四十四、四十五、四十六、四十七、四十八、四十九、五十、五十一、五十二、五十三、五十四、五十五、五十六、五十七、五十八、五十九、六十、六十一、六十二、六十三、六十四、六十五、六十六、六十七、六十八、六十九、七十、七十一、七十二、七十三、七十四、七十五、七十六、七十七、七十八、七十九、八十、八十一、八十二、八十三、八十四、八十五、八十六、八十七、八十八、八十九、九十、九十一、九十二、九十三、九十四、九十五、九十六、九十七、九十八、九十九、一百。

2
 3
 4
 5
 6
 7
 8
 9
 10
 11

● 劉 一 一 ●

— 2 —

4 A 0 4 5 6 7 8 9

五 十 七 年

2
 3
 4
 5
 6
 7
 8
 9
 10
 11
 12

Ratio Readings.

Circuit #5

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------|
| 10.0 | 0.61 | 13.5 | 0.61 |
| 22.0 | 1.24 | 24.5 | 1.24 |
| 40.0 | 2.12 | 41.6 | 2.12 |
| 60.0 | 3.10 | 61.2 | 3.13 |
| 80.0 | 4.16 | 82.0 | 4.22 |
| 93.0 | 4.88 | 94.2 | 4.92 |

Circuit #6

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------|
| 10.0 | 0.59 | 13.5 | 0.59 |
| 22.0 | 1.23 | 24.5 | 1.22 |
| 40.0 | 2.10 | 41.0 | 2.10 |
| 60.0 | 3.08 | 61.2 | 3.11 |
| 80.0 | 4.11 | 82.0 | 4.16 |
| 92.0 | 4.74 | 93.3 | 4.78 |

Circuit #7

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------------------|
| 10.0 | 0.65 | 13.5 | 0.65 |
| 22.0 | 1.23 | 24.5 | 1.23 ^v |
| 40.0 | 2.12 | 41.0 | 2.12 |
| 60.0 | 3.13 | 61.2 | 3.15 |
| 80.0 | 4.18 | 82.0 | 4.25 |
| 95.0 | 5.0 | 96.2 | 5.01 |

Circuit #8

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------|
| 10.0 | 0.60 | 13.5 | 0.60 |
| 22.0 | 1.25 | 24.5 | 1.23 |
| 40.0 | 2.09 | 41.0 | 2.10 |
| 60.0 | 3.09 | 61.2 | 3.12 |
| 80.0 | 4.17 | 82.0 | 4.23 |
| 95.0 | 4.96 | 96.2 | 4.98 |

Circuit #10

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------|
| 10.0 | 0.60 | 13.5 | 0.60 |
| 20.0 | 1.09 | 22.8 | 1.09 |
| 40.0 | 2.08 | 41.0 | 2.10 |
| 60.0 | 3.05 | 61.2 | 3.09 |
| 80.0 | 4.05 | 82.0 | 4.10 |
| 90.0 | 4.64 | 91.3 | 4.69 |
| 95.0 | 4.95 | 96.2 | 4.97 |

Circuit #11

| I_H | I_1 | I_P | I_S |
|-------|-------|-------|-------|
| 20.0 | 1.08 | 22.8 | 1.08 |
| 40.0 | 2.08 | 41.0 | 2.10 |
| 60.0 | 3.09 | 61.2 | 3.13 |
| 80.0 | 4.14 | 82.0 | 4.17 |
| 90.0 | 4.64 | 91.3 | 4.69 |
| 95.0 | 4.95 | 96.2 | 4.97 |

Ratio Readings.

Circuit #12.

Circuit #13.

| I_H | I_2 | I_P | I_S | I_H | I_2 | I_P | I_S |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 10.0 | 0.600 | 13.50 | 0.600 | 10.0 | 0.600 | 13.50 | 0.600 |
| 20.0 | 1.146 | 22.80 | 1.125 | 22.0 | 1.220 | 24.50 | 1.210 |
| 30.0 | 2.100 | 41.80 | 2.100 | 40.0 | 2.050 | 41.00 | 2.050 |
| 50.0 | 3.065 | 61.20 | 3.095 | 60.0 | 3.055 | 61.20 | 3.080 |
| 80.0 | 4.070 | 82.00 | 4.120 | 80.0 | 4.060 | 82.00 | 4.110 |
| 95.0 | 4.900 | 96.20 | 4.920 | 93.0 | 4.810 | 94.20 | 4.840 |

Resistance #12.

| I | E | #I | #E | R |
|---|-------|------|-------|-------|
| 1 | 0.222 | 0.99 | 0.210 | .2125 |
| 2 | 0.430 | 1.98 | 0.420 | .2120 |
| 3 | 0.635 | 2.96 | 0.625 | .2110 |
| 4 | 0.847 | 3.89 | 0.830 | .2130 |
| 5 | 1.055 | 4.86 | 1.030 | .2120 |

Impedance #13.

| I_1 | E_H | Alt. | # I_1 | I_{HW} | I_2 | E | Z |
|-------|-------|-------|---------|----------|-------|-------|------|
| 0.795 | 24.0 | 50.50 | 0.790 | 0.760 | 0.030 | 0.076 | 2.53 |
| 1.283 | 40.0 | 50.50 | 1.280 | 1.240 | .041 | .117 | 2.93 |
| 2.500 | 80.0 | 50.50 | 2.520 | 2.440 | 0.080 | 0.229 | 2.88 |
| 3.100 | 100.0 | 50.50 | 3.125 | 3.000 | 0.125 | 0.280 | 2.29 |



Circuit #1

 $R_s = .0906$ $L = .000346$

| I _{ph} | I ₂ | Defl. | K | I _{#ph} | #I _s | Sin.a | I _p | R | Alpha | |
|-----------------|----------------|-------|-------|------------------|-----------------|-------|----------------|-------|-------|-------|
| | | | | | | | | | ° | ' |
| 4.49 | 0.20 | 4.0 | 76.10 | 4.55 | 0.180 | .0643 | 1.8 | 10.00 | 3 | 41.2 |
| 4.54 | 0.30 | 7.5 | 79.00 | 4.60 | 0.288 | .0717 | 6.0 | 20.83 | 4 | 06.7 |
| 4.48 | 0.62 | 12.0 | 80.80 | 4.54 | 0.525 | .0623 | 11.2 | 21.32 | 3 | 34.3 |
| 4.46 | 0.85 | 14.0 | 81.40 | 4.52 | 0.850 | .0448 | 18.0 | 21.18 | 2 | 34.0 |
| 4.44 | 1.0 | 16.0 | 81.80 | 4.50 | 1.000 | .0435 | 21.1 | 21.10 | 2 | 29.5 |
| 4.47 | 1.18 | 18.5 | 82.00 | 4.53 | 1.190 | .0418 | 25.1 | 21.10 | 2 | 23.7 |
| 4.42 | 1.33 | 21.0 | 82.70 | 4.485 | 1.338 | .0422 | 28.2 | 21.08 | 2 | 25.0 |
| 4.41 | 1.47 | 23.2 | 83.00 | 4.48 | 1.476 | .0422 | 31.0 | 21.00 | 2 | 25.0 |
| 4.44 | 1.63 | 25.0 | 83.20 | 4.50 | 1.650 | .0405 | 34.4 | 20.84 | 2 | 19.3 |
| 4.53 | 1.72 | 27.5 | 83.50 | 4.58 | 1.738 | .0413 | 36.0 | 20.70 | 2 | 22.0 |
| 4.43 | 1.83 | 29.0 | 83.65 | 4.49 | 1.850 | .0417 | 38.1 | 20.58 | 2 | 23.3 |
| 4.49 | 1.94 | 30.0 | 83.75 | 4.55 | 1.960 | .0402 | 40.1 | 20.45 | 2 | 18.25 |
| 4.48 | 2.05 | 33.0 | 84.00 | 4.54 | 2.050 | .0422 | 42.1 | 20.50 | 2 | 25.0 |
| 4.38 | 2.22 | 33.5 | 84.05 | 4.45 | 2.250 | .0399 | 46.0 | 20.45 | 2 | 17.2 |
| 4.48 | 2.32 | 37.5 | 84.35 | 4.54 | 2.350 | .0417 | 48.0 | 20.41 | 2 | 23.3 |
| 4.41 | 2.50 | 39.3 | 84.45 | 4.478 | 2.530 | .0412 | 51.4 | 20.30 | 2 | 21.6 |
| 4.43 | 2.73 | 42.0 | 84.50 | 4.49 | 2.765 | .0400 | 55.6 | 20.10 | 2 | 17.5 |
| 4.40 | 2.98 | 45.0 | 84.55 | 4.46 | 3.015 | .0396 | 60.6 | 20.07 | 2 | 16.2 |
| 4.42 | 3.22 | 49.5 | 84.55 | 4.48 | 3.265 | .0400 | 65.4 | 20.04 | 2 | 17.5 |
| 4.43 | 3.55 | 53.5 | 84.50 | 4.49 | 3.600 | .0392 | 72.0 | 20.00 | 2 | 14.8 |
| 4.41 | 3.87 | 56.0 | 84.45 | 4.48 | 3.925 | .0378 | 78.0 | 19.89 | 2 | 10.0 |
| 4.42 | 4.23 | 61.5 | 84.35 | 4.48 | 4.285 | .0379 | 85.0 | 19.81 | 2 | 10.3 |
| 4.46 | 4.57 | 65.4 | 84.30 | 4.52 | 4.650 | .0371 | 91.3 | 19.70 | 2 | 07.2 |

1. The first part of the document discusses the importance of maintaining accurate records of all transactions. It emphasizes that proper record-keeping is essential for the transparency and accountability of the organization. This section also outlines the specific procedures for recording and verifying financial data.

2. The second part of the document focuses on the role of the audit committee. It describes the committee's responsibilities in overseeing the internal control system and ensuring that the financial statements are free from material misstatements. The committee is also responsible for monitoring the effectiveness of the internal audit function.

3. The third part of the document addresses the issue of risk management. It explains how the organization identifies, assesses, and mitigates various risks that could impact its financial performance. This section highlights the importance of a proactive risk management approach and the need for regular risk assessments.

4. The fourth part of the document discusses the importance of communication and reporting. It outlines the requirements for timely and accurate reporting of financial information to the board of directors and other stakeholders. This section also emphasizes the need for clear and concise communication of the organization's financial position and performance.

5. The fifth part of the document provides a summary of the key findings and recommendations from the audit. It identifies areas where the organization's internal controls are effective and areas where improvements are needed. The recommendations are designed to help the organization strengthen its internal control system and enhance its financial reporting process.

Circuit #3

 $R_v = .206$ $L = .001074$

| I_{ph} | I_L | Defl. | K | # I_{ph} | # I_L | Sin.a | I_P | R | Alpha |
|----------|-------|-------|-------|------------|---------|-------|-------|-------|--------|
| 4.45 | 0.20 | 6.0 | 78.20 | 4.50 | 0.180 | .0944 | 2.25 | 12.50 | 5 25.2 |
| 4.44 | 0.40 | 11.0 | 80.40 | 4.50 | 0.390 | .0779 | 9.00 | 23.10 | 4 28.0 |
| 4.45 | 0.63 | 14.0 | 81.22 | 4.51 | 0.65 | .0612 | 13.8 | 22.10 | 3 30.2 |
| 4.46 | 0.87 | 17.0 | 81.90 | 4.51 | 0.870 | .0530 | 19.0 | 21.85 | 3 02.3 |
| 4.46 | 1.11 | 19.8 | 82.40 | 4.51 | 1.112 | .0478 | 24.0 | 21.55 | 2 34.5 |
| 4.44 | 1.28 | 21.5 | 82.70 | 4.50 | 1.285 | .0450 | 27.2 | 21.15 | 2 33.0 |
| 4.46 | 1.50 | 25.0 | 83.15 | 4.51 | 1.511 | .0443 | 31.2 | 20.80 | 2 32.4 |
| 4.46 | 1.67 | 27.0 | 83.40 | 4.51 | 1.690 | .0425 | 35.2 | 20.82 | 2 26.1 |
| 4.47 | 1.98 | 30.8 | 83.85 | 4.52 | 2.000 | .0406 | 40.9 | 20.45 | 2 19.6 |
| 4.48 | 2.42 | 35.5 | 84.33 | 4.53 | 2.450 | .0379 | 49.5 | 20.20 | 2 10.3 |
| 4.47 | 2.65 | 39.2 | 84.40 | 4.52 | 2.675 | .0384 | 53.8 | 20.10 | 2 12.0 |
| 4.49 | 3.03 | 42.5 | 84.50 | 4.54 | 3.075 | .0360 | 61.1 | 19.85 | 2 03.8 |
| 4.48 | 3.57 | 48.0 | 84.60 | 4.53 | 3.520 | .0346 | 71.5 | 19.70 | 1 59.0 |
| 4.31 | 3.90 | 50.0 | 84.58 | 4.39 | 3.960 | .0339 | 77.5 | 19.55 | 1 56.7 |
| 4.37 | 4.30 | 55.0 | 84.50 | 4.43 | 4.350 | .0337 | 84.5 | 19.40 | 1 56.0 |
| 4.45 | 4.63 | 57.0 | 84.48 | 4.50 | 4.675 | .0320 | 90.6 | 19.37 | 1 50.0 |
| 4.40 | 5.00 | 65.3 | 84.32 | 4.50 | 5.000 | .0334 | 96.5 | 19.30 | 1 54.2 |

Circuit #4.

 $R_s = .3346$ $L = .003586$

| I_{Ph} | I_z | Defl. | K | # I_{Ph} | # I_s | Sin. a | I_p | R | Alpha |
|----------|-------|-------|-------|------------|---------|--------|-------|-------|--------|
| 4.60 | 0.30 | 9.0 | 79.75 | 4.63 | 0.288 | .0843 | 6.0 | 20.84 | 4 50.2 |
| 4.62 | 0.75 | 14.8 | 81.40 | 4.65 | 0.745 | .0525 | 15.5 | 20.81 | 3 00.5 |
| 4.68 | 0.98 | 16.5 | 81.80 | 4.70 | 0.980 | .0437 | 20.6 | 21.02 | 2 30.3 |
| 4.62 | 1.28 | 21.0 | 82.60 | 4.65 | 1.285 | .0427 | 27.2 | 21.16 | 2 26.8 |
| 4.60 | 1.55 | 24.0 | 83.05 | 4.63 | 1.560 | .0400 | 32.0 | 20.50 | 2 17.5 |
| 4.60 | 1.88 | 27.8 | 83.50 | 4.63 | 1.900 | .0378 | 38.5 | 20.25 | 2 10.0 |
| 4.52 | 2.17 | 31.5 | 83.90 | 4.57 | 2.200 | .0376 | 44.3 | 20.18 | 2 05.8 |
| 4.60 | 2.38 | 33.5 | 84.00 | 4.63 | 2.410 | .0346 | 48.2 | 19.98 | 1 59.0 |
| 4.70 | 2.60 | 39.5 | 84.40 | 4.72 | 2.825 | .0362 | 56.5 | 20.00 | 2 01.0 |
| 4.71 | 3.28 | 45.6 | 84.56 | 4.73 | 3.325 | .0342 | 65.5 | 19.71 | 1 57.6 |
| 4.72 | 3.60 | 47.5 | 84.58 | 4.74 | 3.640 | .0328 | 71.5 | 19.64 | 1 52.8 |
| 4.73 | 3.92 | 53.0 | 84.55 | 4.75 | 3.975 | .0332 | 78.0 | 19.61 | 1 54.2 |
| 4.73 | 4.42 | 58.0 | 84.45 | 4.75 | 4.475 | .0324 | 87.0 | 19.44 | 1 51.4 |
| 4.72 | 4.75 | 62.5 | 84.35 | 4.74 | 4.80 | .0325 | 93.0 | 19.37 | 1 51.7 |

Circuit #5.

 $R_p = .3546$ $L = .0058$

| I_{ph} | I_z | Defl. | K | # I_{ph} | # I_s | Sin.a | I_p | R | Al ha |
|----------|-------|-------|-------|------------|---------|-------|-------|-------|--------|
| 4.87 | 0.30 | 14.5 | 81.22 | 4.87 | 0.29 | .1265 | 6.0 | 20.70 | 7 16.0 |
| 4.91 | 0.85 | 19.5 | 82.35 | 4.90 | 0.85 | .0570 | 17.20 | 20.25 | 3 16.0 |
| 4.91 | 1.27 | 25.0 | 83.18 | 4.90 | 1.27 | .0483 | 25.50 | 20.05 | 2 46.0 |
| 4.90 | 1.80 | 32.2 | 83.40 | 4.89 | 1.80 | .0455 | 35.60 | 19.78 | 2 29.0 |
| 4.90 | 2.55 | 40.0 | 84.42 | 4.89 | 2.56 | .0412 | 42.20 | 19.55 | 2 22.0 |
| 4.90 | 3.14 | 49.6 | 84.60 | 4.89 | 3.16 | .0379 | 61.60 | 19.50 | 2 10.0 |
| 4.88 | 3.58 | 55.5 | 84.50 | 4.88 | 3.62 | .0372 | 70.50 | 19.50 | 2 08.0 |
| 4.87 | 4.12 | 61.0 | 84.40 | 4.87 | 4.17 | .0357 | 81.00 | 19.40 | 2 02.8 |
| 4.83 | 4.40 | 65.0 | 84.30 | 4.83 | 4.45 | .0358 | 86.00 | 19.30 | 2 03.2 |
| 4.82 | 4.75 | 70.8 | 84.20 | 4.82 | 4.78 | .0365 | 92.00 | 19.20 | 2 06.0 |

Circuit #6.

 $R_p = .3546$ $L = .0228$

| I_{ph} | I_z | Defl. | K | # I_{ph} | # I_s | Sin.a | I_p | R | Alpha |
|----------|-------|-------|-------|------------|---------|-------|-------|-------|--------|
| 4.90 | 0.30 | 8.2 | 79.40 | 4.89 | 0.29 | .0729 | 6.5 | 22.40 | 4 11.0 |
| 4.92 | 0.78 | 12.0 | 80.70 | 4.91 | 0.77 | .0390 | 16.5 | 21.20 | 2 15.0 |
| 4.88 | 1.37 | 15.0 | 81.48 | 4.87 | 1.37 | .0276 | 27.2 | 20.10 | 1 35.0 |
| 4.88 | 1.82 | 18.8 | 82.25 | 4.87 | 1.82 | .0258 | 36.0 | 19.78 | 1 29.0 |
| 4.89 | 2.15 | 22.0 | 82.73 | 4.88 | 2.16 | .0251 | 42.2 | 19.53 | 1 26.8 |
| 4.88 | 2.64 | 28.8 | 83.65 | 4.87 | 2.65 | .0267 | 51.0 | 19.63 | 1 32.0 |
| 4.88 | 3.08 | 31.8 | 83.95 | 4.87 | 3.10 | .0250 | 61.0 | 19.65 | 1 26.0 |
| 4.83 | 3.53 | 36.0 | 84.25 | 4.83 | 3.56 | .0248 | 70.2 | 19.70 | 1 25.0 |
| 4.83 | 4.00 | 41.0 | 84.50 | 4.83 | 4.05 | .0249 | 79.7 | 19.65 | 1 26.0 |
| 4.83 | 4.48 | 47.0 | 84.58 | 4.83 | 4.52 | .0254 | 88.5 | 19.52 | 1 27.3 |
| 4.85 | 4.67 | 49.0 | 84.60 | 4.85 | 4.70 | .0255 | 91.5 | 19.45 | 1 27.6 |

Circuit #7.

R_s .1287

L = .000346

| I _{ph} | I ₂ | Defl. | K | #I _{ph} | #I _s | Sin.a | I _p | R | Alpha |
|-----------------|----------------|-------|-------|------------------|-----------------|-------|----------------|-------|---------|
| 4.91 | 0.35 | 11.5 | 80.60 | 4.900 | 0.35 | .0835 | 7.3 | 20.90 | 4 48.0 |
| 4.90 | 0.88 | 21.0 | 82.62 | 4.890 | 1.28 | .0497 | 25.6 | 20.00 | 2 51.0 |
| 4.89 | 1.67 | 31.0 | 83.85 | 4.880 | 1.68 | .0450 | 33.3 | 19.80 | 2 35.0 |
| 4.88 | 2.00 | 35.5 | 84.23 | 4.875 | 2.00 | .0432 | 39.0 | 19.50 | 2 29.0 |
| 4.87 | 2.38 | 41.5 | 84.50 | 4.865 | 2.40 | .0421 | 46.5 | 19.35 | 2 25.0 |
| 4.88 | 2.90 | 49.0 | 84.60 | 4.875 | 2.93 | .0406 | 57.0 | 19.45 | 2 19.5 |
| 4.82 | 3.32 | 54.0 | 84.55 | 4.820 | 3.37 | .0395 | 65.5 | 19.40 | 2 15.1 |
| 4.80 | 3.70 | 59.0 | 84.45 | 4.805 | 3.75 | .0383 | 72.5 | 19.32 | 2 13.0 |
| 4.80 | 4.00 | 62.5 | 84.35 | 4.805 | 4.05 | .0380 | 78.2 | 19.30 | 2 10.6 |
| 4.80 | 4.48 | 69.5 | 84.25 | 4.805 | 4.52 | .0379 | 87.2 | 19.28 | 2 10.31 |
| 4.78 | 4.88 | 73.5 | 84.18 | 4.850 | 4.92 | .0366 | 94.5 | 19.20 | 2 05.9 |

Circuit #8

R_s .2292

L = .000346

| I _{ph} | I ₂ | Defl. | K | #I _{ph} | #I _s | Sin.a | I _p | R | Alpha |
|-----------------|----------------|-------|-------|------------------|-----------------|-------|----------------|-------|--------|
| 4.93 | 0.35 | 13.0 | 81.00 | 4.915 | 0.35 | .0931 | 7.8 | 22.30 | 5 21.0 |
| 4.88 | 0.88 | 19.0 | 82.28 | 4.875 | 0.88 | .0538 | 18.2 | 20.70 | 3 05.0 |
| 4.91 | 1.33 | 25.0 | 83.15 | 4.900 | 1.33 | .0461 | 27.0 | 20.30 | 2 38.0 |
| 4.91 | 1.70 | 31.0 | 83.85 | 4.900 | 1.70 | .0444 | 34.0 | 20.00 | 2 33.0 |
| 4.91 | 2.13 | 37.5 | 84.33 | 4.900 | 2.14 | .0424 | 42.0 | 19.60 | 2 26.0 |
| 4.91 | 2.55 | 41.0 | 84.48 | 4.900 | 2.56 | .0387 | 50.2 | 19.60 | 2 13.0 |
| 4.90 | 3.00 | 46.8 | 84.58 | 4.890 | 3.02 | .0374 | 59.0 | 19.54 | 2 09.0 |
| 4.89 | 3.50 | 54.5 | 84.53 | 4.880 | 3.54 | .0373 | 69.3 | 19.55 | 2 08.0 |
| 4.90 | 4.00 | 62.0 | 84.37 | 4.890 | 4.05 | .0371 | 78.8 | 19.45 | 2 07.0 |
| 4.89 | 4.52 | 68.0 | 84.25 | 4.880 | 4.93 | .0335 | 95.5 | 19.35 | 1 55.0 |
| 4.90 | 4.925 | 73.5 | 84.18 | 4.890 | 4.94 | .0361 | 95.6 | 19.35 | 2 04.0 |

Circuit #10

R_g .259

L = .000346

| I _{ph} | I ₂ | DeKl. | K | #I _{ph} | #I _s | Sin.a | I _p | R | Alpha |
|-----------------|----------------|-------|-------|------------------|-----------------|-------|----------------|-------|--------|
| 5.00 | 0.35 | 16.0 | 81.70 | 4.98 | 0.350 | .1121 | 7.5 | 21.40 | 6 26.2 |
| 4.95 | 0.62 | 21.2 | 82.65 | 4.94 | 0.61 | .0847 | 13.2 | 21.40 | 4 59.5 |
| 4.92 | 1.04 | 27.0 | 83.40 | 4.91 | 1.04 | .0635 | 22.0 | 21.20 | 3 38.5 |
| 4.94 | 1.22 | 28.0 | 83.55 | 4.93 | 1.23 | .0554 | 26.0 | 21.20 | 3 10.6 |
| 4.91 | 1.52 | 33.0 | 84.05 | 4.90 | 1.53 | .0525 | 31.5 | 20.60 | 3 00.5 |
| 4.85 | 1.82 | 35.5 | 84.33 | 4.85 | 1.80 | .0482 | 37.0 | 20.50 | 2 46.0 |
| 4.91 | 2.03 | 38.5 | 84.40 | 4.90 | 2.04 | .0457 | 42.0 | 20.55 | 2 37.0 |
| 4.92 | 2.25 | 40.2 | 84.45 | 4.91 | 2.29 | .0423 | 46.5 | 20.30 | 2 25.6 |
| 4.91 | 2.51 | 43.5 | 84.55 | 4.90 | 2.54 | .0413 | 51.2 | 20.15 | 2 22.0 |
| 4.92 | 2.73 | 46.3 | 84.58 | 4.91 | 2.79 | .0398 | 56.0 | 20.05 | 2 17.0 |
| 4.93 | 2.98 | 48.5 | 84.60 | 4.92 | 3.02 | .0387 | 60.0 | 19.90 | 2 13.0 |
| 4.92 | 3.23 | 53.0 | 84.55 | 4.91 | 3.28 | .0389 | 65.3 | 19.90 | 2 13.7 |
| 4.91 | 3.52 | 54.5 | 84.50 | 4.90 | 3.57 | .0369 | 70.8 | 19.85 | 2 07.0 |
| 3.96 | 3.50 | 44.6 | 84.55 | 4.09 | 3.55 | .0363 | 70.5 | 19.85 | 2 05.0 |
| 3.96 | 3.76 | 48.3 | 84.60 | 4.09 | 3.81 | .0366 | 75.2 | 19.70 | 2 06.0 |
| 3.92 | 4.01 | 50.0 | 84.58 | 4.06 | 4.05 | .0360 | 79.6 | 19.65 | 2 03.3 |
| 3.90 | 4.20 | 52.0 | 84.55 | 4.04 | 4.25 | .0358 | 83.5 | 19.65 | 2 03.0 |
| 3.88 | 4.50 | 54.2 | 84.52 | 4.02 | 4.55 | .0350 | 88.0 | 19.55 | 2 00.0 |
| 3.92 | 4.67 | 57.0 | 84.40 | 4.06 | 4.725 | .0352 | 92.0 | 19.45 | 2 01.0 |
| 3.92 | 4.95 | 59.0 | 84.40 | 4.06 | 4.99 | .0346 | 97.0 | 19.40 | 1 59.0 |

Circuit #11

R_g .3546

L = .009626

| I _{ph} | I ₂ | Defl. | K | #I _{ph} | #I _s | Sin.a | I _p | R | Alpha |
|-----------------|----------------|-------|-------|------------------|-----------------|-------|----------------|-------|--------|
| 4.91 | 0.58 | 13.5 | 81.10 | 4.90 | 0.575 | .0592 | 13.0 | 22.60 | 3 23.6 |
| 4.92 | 1.00 | 19.2 | 82.30 | 4.91 | 1.000 | .0475 | 21.5 | 21.50 | 2 43.3 |
| 4.87 | 1.52 | 23.5 | 82.98 | 4.87 | 1.463 | .0398 | 30.8 | 21.05 | 2 16.9 |
| 4.94 | 2.03 | 29.5 | 83.70 | 4.93 | 2.040 | .0350 | 41.8 | 20.50 | 202.0 |
| 4.96 | 2.55 | 37.0 | 84.30 | 4.95 | 2.530 | .0338 | 51.5 | 20.20 | 1 59.6 |
| 4.96 | 2.95 | 41.5 | 84.50 | 4.95 | 2.988 | .0332 | 59.8 | 20.00 | 1 54.3 |
| 4.86 | 3.54 | 48.0 | 84.60 | 4.86 | 3.585 | .0326 | 71.0 | 19.80 | 1 52.0 |
| 4.90 | 4.00 | 52.0 | 84.57 | 4.89 | 4.060 | .0309 | 79.8 | 19.65 | 1 46.2 |
| 4.88 | 4.50 | 59.5 | 84.40 | 4.88 | 4.525 | .0319 | 88.5 | 19.55 | 1 49.7 |

Circuit #12.

 $R_s = .212$ $L = .000346$

| I_{ph} | I_s | Defl. | K | # I_{ph} | # I_s | Sin.a | I_p | R | Theta ° / |
|----------|-------|-------|-------|------------|---------|-------|-------|-------|--------------|
| 4.92 | 0.35 | 10.0 | 80.13 | 4.90 | 0.35 | .0728 | 7.5 | 21.40 | 4 10.0 |
| 4.90 | 0.80 | 16.5 | 81.80 | 4.89 | 0.80 | .0518 | 16.7 | 21.00 | 2 58.0 |
| 4.89 | 1.32 | 23.5 | 82.98 | 4.88 | 1.32 | .0440 | 27.2 | 20.62 | 2 31.0 |
| 4.92 | 1.67 | 28.5 | 83.60 | 4.90 | 1.69 | .0411 | 34.5 | 20.40 | 2 21.0 |
| 4.90 | 2.00 | 33.0 | 84.03 | 4.89 | 2.00 | .0401 | 40.5 | 20.25 | 2 18.0 |
| 4.91 | 2.57 | 40.0 | 84.44 | 4.90 | 2.58 | .0375 | 51.8 | 20.08 | 2 09.0 |
| 4.90 | 3.00 | 46.0 | 84.58 | 4.89 | 3.02 | .0368 | 60.2 | 19.93 | 2 06.5 |
| 4.91 | 3.51 | 51.5 | 84.58 | 4.90 | 3.55 | .0350 | 70.5 | 19.85 | 2 01.0 |
| 4.80 | 4.02 | 57.0 | 84.49 | 4.80 | 4.07 | .0345 | 80.8 | 19.85 | 1 58.5 |
| 4.90 | 4.50 | 65.0 | 84.30 | 4.89 | 4.55 | .0346 | 89.6 | 19.68 | 1 59.0 |
| 4.88 | 4.97 | 70.0 | 84.22 | 4.87 | 4.99 | .0342 | 97.8 | 19.60 | 1 57.5 |

Circuit#13.

 $R_s = .3546$ $L = .0166$

| I_{ph} | I_s | Defl. | K | # I_{ph} | # I_s | Sin.a | I_p | R | Theta ° / |
|----------|-------|-------|-------|------------|---------|-------|-------|-------|--------------|
| 4.91 | 0.35 | 7.3 | 79.00 | 4.90 | 0.35 | .0538 | 7.5 | 21.40 | 3 03.0 |
| 4.86 | 0.85 | 13.8 | 81.20 | 4.86 | 0.85 | .0412 | 18.0 | 21.18 | 2 22.0 |
| 4.88 | 1.28 | 19.5 | 82.37 | 4.87 | 1.29 | .0378 | 26.8 | 20.85 | 2 10.0 |
| 4.88 | 1.28 | 22.5 | 82.32 | 4.87 | 1.65 | .0338 | 34.0 | 20.62 | 1 56.0 |
| 4.88 | 1.98 | 26.0 | 83.30 | 4.87 | 2.00 | .0321 | 40.8 | 20.42 | 1 50.0 |
| 4.87 | 2.41 | 30.5 | 83.81 | 4.86 | 2.42 | .0310 | 48.8 | 20.22 | 1 47.0 |
| 4.88 | 3.03 | 38.6 | 84.40 | 4.87 | 3.05 | .0308 | 61.0 | 20.00 | 1 46.0 |
| 4.88 | 3.55 | 43.5 | 84.52 | 4.87 | 3.58 | .0295 | 70.0 | 19.55 | 1 41.0 |
| 4.87 | 3.98 | 50.8 | 84.58 | 4.86 | 4.03 | .0307 | 79.5 | 19.70 | 1 45.0 |
| 4.85 | 4.50 | 54.5 | 84.52 | 4.85 | 4.55 | .0291 | 89.0 | 19.56 | 1 40.0 |
| 4.81 | 4.80 | 57.5 | 83.96 | 4.81 | 4.82 | .0296 | 94.0 | 19.50 | 1 42.0 |

Circuit #1.

| I _p | Ratio | Alpha ° / | Ratio Error | Angle Error. | | | Total Error. | | |
|----------------|-------|--------------|----------------|--------------|--------------|--------------|--------------|--------------|--------------|
| | | | | 100% PF. | 86.7% PF. | 84.3% PF. | 100% PF. | 86.7% PF. | 84.3% PF. |
| 10 | 21.30 | 3 27.0 | 6.50 | .181 | 3.70 | 7.45 | 6.681 | 10.2 | 13.95 |
| 20 | 21.15 | 2 34.0 | 5.75 | .100 | 2.75 | 5.55 | 5.850 | 8.5 | 11.30 |
| 30 | 20.95 | 2 23.0 | 4.75 | .087 | 2.50 | 5.25 | 4.837 | 7.25 | 10.00 |
| 40 | 20.60 | 2 20.0 | 3.00 | .083 | 2.50 | 5.20 | 3.083 | 5.5 | 8.20 |
| 50 | 20.35 | 2 18.0 | 1.75 | .081 | 2.40 | 5.00 | 1.831 | 4.2 | 6.75 |
| 60 | 20.15 | 2 15.5 | 0.75 | .073 | 2.30 | 4.90 | 0.828 | 3.0 | 5.65 |
| 70 | 20.00 | 2 13.0 | 0.00 | .075 | 2.30 | 4.75 | 0.075 | 2.30 | 4.75 |
| 80 | 19.90 | 2 11.3 | -0.50 | .073 | 2.25 | 4.10 | -0.427 | 1.8 | 4.20 |
| 90 | 19.72 | 2 09.0 | -1.40 | .069 | 2.15 | 4.60 | -1.331 | 0.9 | 3.20 |
| 100 | 19.50 | 2 07.0 | -2.50 | .068 | 2.20 | 4.50 | -2.432 | -0.30 | 2.00 |

Circuit #3.

| I _p | Ratio | Alpha ° / | Ratio Error | Angle Error. | | | Total Error. | | |
|----------------|-------|--------------|----------------|--------------|--------------|--------------|--------------|--------------|--------------|
| | | | | 100% PF. | 86.7% PF. | 84.3% PF. | 100% PF. | 86.7% PF. | 84.3% PF. |
| 10 | 22.85 | 3 54.0 | 14.25 | .232 | 4.30 | 8.30 | 14.482 | 18.55 | 22.55 |
| 20 | 21.60 | 2 58.0 | 8.0 | .134 | 3.10 | 5.55 | 8.134 | 11.10 | 14.55 |
| 30 | 20.92 | 2 32.0 | 4.60 | .092 | 2.70 | 5.35 | 4.692 | 7.30 | 9.95 |
| 40 | 20.50 | 2 19.0 | 2.50 | .082 | 2.50 | 4.90 | 2.582 | 5.00 | 7.40 |
| 50 | 20.20 | 2 10.0 | 1.00 | .071 | 2.40 | 4.50 | 1.071 | 3.40 | 5.50 |
| 60 | 19.92 | 2 03.5 | -0.40 | .063 | 2.25 | 4.30 | -.337 | 1.85 | 3.90 |
| 70 | 19.70 | 1 59.0 | -1.50 | .060 | 2.20 | 4.20 | -1.440 | 0.70 | 2.70 |
| 80 | 19.50 | 1 55.5 | -2.50 | .056 | 2.15 | 4.10 | -2.444 | -0.35 | 1.60 |
| 90 | 19.36 | 1 53.0 | -3.20 | .054 | 2.05 | 3.90 | -3.146 | -1.15 | 0.70 |
| 100 | 19.28 | 1 51.0 | -3.60 | .052 | 2.00 | 3.80 | -3.548 | -1.60 | 0.20 |

Circuit #4.

| I _p | Ratio | Alpha ° / | Ratio Error | Angle Error. | | | Total Error. | | |
|----------------|-------|--------------|----------------|--------------|--------------|--------------|--------------|--------------|--------------|
| | | | | 100% PF. | 86.7% PF. | 84.3% PF. | 100% PF. | 86.7% PF. | 84.3% PF. |
| 10 | 21.02 | 3 36.5 | 15.10 | .198 | 4.00 | 7.65 | 5.298 | 9.10 | 12.75 |
| 20 | 20.70 | 2 44.0 | 3.50 | .114 | 3.90 | 6.50 | 3.614 | 7.40 | 10.00 |
| 30 | 20.41 | 2 20.5 | 2.05 | .083 | 3.50 | 5.00 | 2.133 | 5.55 | 7.05 |
| 40 | 20.16 | 2 08.5 | 0.80 | .069 | 3.130 | 4.50 | 0.869 | 4.10 | 5.30 |
| 50 | 19.95 | 2 01.0 | -0.25 | .062 | 3.20 | 4.30 | -0.188 | 2.95 | 4.05 |
| 60 | 19.79 | 1 56.0 | -1.07 | .057 | 3.15 | 4.20 | -1.013 | 2.08 | 3.13 |
| 70 | 19.68 | 1 54.0 | -1.60 | .055 | 3.10 | 4.10 | -1.545 | 1.50 | 2.50 |
| 80 | 19.63 | 1 52.0 | -1.85 | .053 | 3.05 | 3.90 | -1.797 | 1.20 | 2.05 |
| 90 | 19.62 | 1 52.0 | -1.90 | .053 | 3.05 | 3.90 | -1.847 | 1.15 | 2.00 |
| 100 | 19.62 | 1 52.0 | -1.90 | .053 | 3.05 | 3.90 | -1.847 | 1.15 | 2.00 |

Circuit #5.

| I | Ratio | Alpha | Ratio Error | Angle Error | | | Total Error | | |
|-----|-------|-------|----------------|-------------|-------|-------|-------------|-------|-------|
| | | | | 100% | 86.7% | 64.3% | 100% | 86.7% | 64.3% |
| I | | ° / | | P.F. | P.F. | P.F. | P.F. | P.F. | P.F. |
| 10 | 20.52 | 3 51 | 2.60 | 0.52 | 6.50 | 12.8 | 3.12 | 9.10 | 15.40 |
| 20 | 20.15 | 3 05 | 0.75 | 0.15 | 3.40 | 6.8 | 0.90 | 4.15 | 7.55 |
| 30 | 19.90 | 2 38 | -0.50 | 0.11 | 3.80 | 5.7 | -0.79 | 2.30 | 5.20 |
| 40 | 19.70 | 2 25 | -1.50 | 0.09 | 2.70 | 5.3 | -1.41 | 1.20 | 3.80 |
| 50 | 19.56 | 2 18 | -2.15 | 0.08 | 2.50 | 5.2 | -2.07 | 0.35 | 3.05 |
| 60 | 19.50 | 2 12 | -2.50 | 0.08 | 2.40 | 5.0 | -2.42 | -0.10 | 2.50 |
| 70 | 19.46 | 2 08 | -2.70 | 0.07 | 2.30 | 4.7 | -2.63 | -0.40 | 2.00 |
| 80 | 19.40 | 2 02 | -3.00 | 0.06 | 2.20 | 4.5 | -2.94 | -0.80 | 1.50 |
| 90 | 19.25 | 1 56 | -3.75 | 0.06 | 2.10 | 4.3 | -3.39 | -1.65 | 0.55 |
| 100 | 19.00 | 1 52 | -5.00 | 0.05 | 2.00 | 4.0 | -4.95 | -3.00 | -1.00 |

Circuit #6

| | | | | | | | | | |
|-----|-------|------|-------|------|------|------|-------|-------|-------|
| 10 | 21.95 | 3 20 | 9.58 | 0.17 | 3.70 | 7.2 | 10.05 | 15.58 | 17.08 |
| 20 | 20.75 | 1 54 | 3.75 | 0.06 | 2.00 | 4.3 | 3.81 | 5.75 | 8.05 |
| 30 | 19.90 | 1 33 | -0.50 | 0.04 | 1.80 | 3.5 | -0.46 | 1.30 | 3.00 |
| 40 | 19.70 | 1 27 | 1.50 | 0.03 | 1.70 | 3.2 | -1.47 | 0.20 | 1.70 |
| 50 | 19.63 | 1 26 | -1.85 | 0.03 | 1.60 | 3.0 | -1.82 | -0.25 | 1.15 |
| 60 | 19.65 | 1 26 | -1.75 | 0.03 | 1.60 | 3.00 | -1.72 | -0.15 | 1.25 |
| 70 | 19.70 | 1 26 | -1.50 | 0.03 | 1.60 | 3.0 | -1.47 | 0.10 | 1.50 |
| 80 | 19.65 | 1 26 | -1.75 | 0.03 | 1.60 | 3.0 | -1.72 | -0.15 | 1.25 |
| 90 | 19.50 | 1 27 | -2.50 | 0.03 | 1.70 | 3.2 | -2.47 | -0.80 | 0.07 |
| 100 | 19.30 | 1 28 | -3.50 | 0.03 | 1.80 | 3.3 | -3.47 | -1.70 | -0.20 |

Circuit #7.

| | | | | | | | | | |
|-----|-------|------|-------|------|------|-----|-------|-------|-------|
| 10 | 20.70 | 4 24 | 3.50 | 0.19 | 4.80 | 9.5 | 3.79 | 8.30 | 13.00 |
| 20 | 20.15 | 3 12 | 0.75 | 0.16 | 3.50 | 6.7 | 0.91 | 4.25 | 7.45 |
| 30 | 19.85 | 2 41 | -0.75 | 0.11 | 3.00 | 5.8 | -0.64 | 2.25 | 5.05 |
| 40 | 19.65 | 2 28 | -1.75 | 0.09 | 2.70 | 5.3 | -1.66 | 0.95 | 3.55 |
| 50 | 19.52 | 2 22 | -2.40 | 0.09 | 2.50 | 5.2 | -2.31 | 0.10 | 2.80 |
| 60 | 19.41 | 2 18 | -2.95 | 0.08 | 2.50 | 5.1 | -2.87 | -0.45 | +2.05 |
| 70 | 19.35 | 2 14 | -3.25 | 0.08 | 2.30 | 4.9 | -3.13 | -0.95 | +1.65 |
| 80 | 19.28 | 2 11 | -3.60 | 0.07 | 2.30 | 4.8 | -3.53 | -1.30 | 1.20 |
| 90 | 19.22 | 2 08 | -3.90 | 0.07 | 2.30 | 4.7 | -3.63 | -1.60 | 0.80 |
| 100 | 19.18 | 2 06 | -4.60 | 0.07 | 2.20 | 4.5 | -4.53 | -2.40 | -0.10 |

Circuit #8.

| | | | | | | | | | |
|-----|-------|------|-------|------|------|------|-------|-------|-------|
| 10 | 21.75 | 4 27 | 8.75 | 0.30 | 4.80 | 9.5 | 9.05 | 13.55 | 18.55 |
| 20 | 20.62 | 3 01 | 3.10 | 0.13 | 3.20 | 6.5 | 3.23 | 5.30 | 9.60 |
| 30 | 20.08 | 2 37 | 0.40 | 0.10 | 2.80 | 5.7 | 0.50 | 3.20 | 6.10 |
| 40 | 19.95 | 2 24 | -0.25 | 0.09 | 2.40 | 5.3 | -0.16 | 2.15 | 5.00 |
| 50 | 19.56 | 2 15 | -2.20 | 0.08 | 2.30 | 4.9 | -2.12 | 0.10 | 2.70 |
| 60 | 19.50 | 2 11 | -2.50 | 0.07 | 2.30 | 4.80 | -2.43 | -0.20 | 2.30 |
| 70 | 19.48 | 2 08 | -2.60 | 0.07 | 2.30 | 4.7 | -2.53 | -0.30 | 2.10 |
| 80 | 19.45 | 2 07 | -2.75 | 0.07 | 2.20 | 4.6 | -2.68 | -0.55 | 1.85 |
| 90 | 19.40 | 2 06 | -3.00 | 0.07 | 2.20 | 4.5 | -2.93 | -0.80 | 1.50 |
| 100 | 19.30 | 2 04 | -3.50 | 0.07 | 2.15 | 4.4 | -3.43 | -1.35 | 0.90 |

Circuit #10.

| I | Ratio | Alpha | Ratio Error | Angle Error | | | Total Error. | | |
|-----|-------|-------|----------------|-------------|-------|-------|--------------|-------|-------|
| | | | | 100% | 86.7% | 64.3% | 100% | 86.7% | 64.3% |
| | | | | P.F. | P.F. | P.F. | P.F. | P.F. | P.F. |
| 10 | 21.50 | 5 44 | 7.50 | .500 | 5.25 | 12.3 | 8.000 | 13.75 | 19.30 |
| 20 | 20.98 | 3 57 | 4.90 | .232 | 4.20 | 8.6 | 5.133 | 9.10 | 13.50 |
| 30 | 20.65 | 3 07 | 3.75 | .148 | 3.25 | 6.7 | 3.898 | 7.00 | 10.45 |
| 40 | 20.37 | 2 39 | 1.85 | .107 | 2.75 | 5.7 | 1.957 | 4.60 | 7.55 |
| 50 | 20.16 | 2 23 | 0.80 | .087 | 2.40 | 5.0 | 0.887 | 3.20 | 5.60 |
| 60 | 19.97 | 2 14 | -0.15 | .075 | 2.25 | 4.8 | -0.075 | 2.10 | 4.60 |
| 70 | 19.80 | 2 09 | -1.00 | .069 | 2.23 | 4.5 | -0.931 | 1.23 | 3.50 |
| 80 | 19.65 | 2 04 | -1.75 | .063 | 2.22 | 4.4 | -1.637 | 0.47 | 2.65 |
| 90 | 19.50 | 2 01 | -2.50 | .062 | 2.20 | 4.4 | -2.438 | -0.30 | 1.90 |
| 100 | 19.35 | 1 59 | -3.25 | .060 | 2.20 | 4.3 | -3.190 | -1.05 | 1.05 |

Circuit #11.

| | | | | | | | | | |
|-----|-------|------|-------|------|------|------|--------|-------|-------|
| 10 | 23.00 | 3 48 | 15.00 | .210 | 4.05 | 8.10 | 15.210 | 19.05 | 23.10 |
| 20 | 21.84 | 2 49 | 9.20 | .121 | 2.95 | 6.6 | 9.321 | 12.15 | 15.80 |
| 30 | 21.06 | 2 19 | 5.30 | .082 | 2.45 | 5.0 | 5.082 | 7.75 | 10.30 |
| 40 | 20.57 | 2 04 | 2.85 | .063 | 2.20 | 4.5 | 2.913 | 5.05 | 7.30 |
| 50 | 20.23 | 1 56 | 1.15 | .057 | 2.15 | 4.3 | 1.207 | 3.30 | 5.45 |
| 60 | 19.99 | 1 54 | -0.05 | .055 | 2.12 | 4.2 | 0.005 | 2.07 | 4.15 |
| 70 | 19.81 | 1 50 | -0.95 | .051 | 2.10 | 4.0 | -0.899 | 1.15 | 3.05 |
| 80 | 19.65 | 1 49 | -1.75 | .050 | 2.00 | 3.9 | -1.700 | 0.25 | 2.15 |
| 90 | 19.55 | 1 49 | -2.25 | .050 | 2.00 | 3.9 | -2.200 | -0.25 | 1.65 |
| 100 | 19.44 | 1 49 | -2.80 | .050 | 2.00 | 3.9 | -2.750 | -0.80 | 1.10 |

Circuit #12.

| | | | | | | | | | |
|-----|-------|------|-------|------|------|-----|--------|-------|-------|
| 10 | 21.29 | 3 39 | 6.45 | .203 | 4.00 | 7.7 | 6.653 | 10.45 | 14.15 |
| 20 | 20.85 | 2 47 | 4.25 | .113 | 2.95 | 5.9 | 4.368 | 7.20 | 10.15 |
| 30 | 20.52 | 2 26 | 2.60 | .090 | 2.55 | 5.2 | 2.690 | 5.15 | 7.75 |
| 40 | 20.25 | 2 15 | 1.25 | .077 | 2.45 | 4.8 | 1.327 | 3.70 | 6.00 |
| 50 | 20.08 | 2 08 | 0.40 | .069 | 2.35 | 4.5 | 0.469 | 2.75 | 4.90 |
| 60 | 19.97 | 2 03 | -0.15 | .065 | 2.20 | 4.3 | -0.086 | 2.05 | 4.15 |
| 70 | 19.86 | 2 00 | -0.70 | .061 | 2.15 | 4.3 | -0.639 | 1.45 | 3.55 |
| 80 | 19.80 | 1 59 | -1.00 | .060 | 2.10 | 4.2 | -0.940 | 1.10 | 3.20 |
| 90 | 19.70 | 1 58 | -1.50 | .059 | 2.05 | 4.2 | -1.441 | 0.55 | 2.65 |
| 100 | 19.57 | 1 57 | -2.15 | .058 | 2.00 | 4.1 | -2.092 | -0.15 | 1.95 |

Circuit #13.

| | | | | | | | | | |
|-----|-------|------|-------|------|------|-----|--------|-------|-------|
| 10 | 21.37 | 2 5 | 6.85 | .125 | 3.00 | 6.0 | 6.975 | 9.85 | 12.85 |
| 20 | 21.09 | 2 20 | 5.45 | .033 | 2.50 | 4.9 | 5.533 | 7.95 | 10.40 |
| 30 | 20.71 | 2 00 | 3.55 | .061 | 2.15 | 4.3 | 3.611 | 5.70 | 7.80 |
| 40 | 20.40 | 1 50 | 2.00 | .051 | 1.90 | 3.6 | 2.051 | 3.90 | 5.60 |
| 50 | 20.15 | 1 47 | 0.80 | .048 | 1.80 | 3.6 | 0.848 | 2.60 | 4.40 |
| 60 | 19.96 | 1 45 | -0.20 | .047 | 1.75 | 3.6 | -0.154 | 1.55 | 3.25 |
| 70 | 19.80 | 1 44 | -1.00 | .046 | 1.74 | 3.5 | -0.954 | 0.74 | 2.54 |
| 80 | 19.66 | 1 43 | -1.70 | .045 | 1.73 | 3.5 | -1.655 | 0.03 | 1.83 |
| 90 | 19.53 | 1 42 | -2.35 | .044 | 1.72 | 3.5 | -2.306 | -0.63 | 1.17 |
| 100 | 19.40 | 1 41 | -3.00 | .043 | 1.70 | 3.5 | -2.957 | -1.30 | 0.50 |

Ratio Readings.
Constant Resistance.

| Circuit | <u>4</u> | <u>5</u> | <u>11</u> | <u>13</u> | <u>6</u> |
|---------|-----------------|-----------------------|-----------------------|-----------|----------|
| I_p | $\frac{20}{70}$ | $\frac{20.15}{21.84}$ | $\frac{21.10}{20.75}$ | | |
| 20 | 20.16 | 19.70 | 20.57 | 20.40 | 19.70 |
| 40 | 19.79 | 19.50 | 19.99 | 19.96 | 19.65 |
| 60 | 19.63 | 19.40 | 19.65 | 19.65 | 19.65 |
| 80 | 19.62 | 19.00 | 19.44 | 19.40 | 19.30 |
| 100 | | | | | |

Constant Reactance.

| Circuit | <u>1</u> | <u>7</u> | <u>12</u> | <u>8</u> | <u>10</u> |
|---------|----------|----------|-----------|----------|-----------|
| 20 | 21.15 | 20.15 | 20.88 | 20.62 | 20.98 |
| 40 | 20.60 | 19.65 | 20.25 | 19.95 | 20.37 |
| 60 | 20.15 | 19.41 | 19.85 | 19.50 | 19.97 |
| 80 | 19.90 | 19.28 | 19.80 | 19.45 | 19.65 |
| 100 | 19.50 | 19.18 | 19.55 | 19.30 | 19.35 |

Angle Readings.

Constant Resistance.

| Circuit | <u>4</u> | <u>5</u> | <u>11</u> | <u>13</u> | <u>6</u> |
|---------|----------|----------|-----------|-----------|----------|
| 20 | 2 44 | 3 05 | 2 20 | 2 49 | 1 54 |
| 40 | 2 09 | 2 25 | 2 04 | 1 50 | 1 27 |
| 60 | 1 56 | 2 12 | 1 54 | 1 45 | 1 26 |
| 80 | 1 52 | 2 02 | 1 49 | 1 43 | 1 27 |
| 100 | 1 52 | 1 52 | 1 49 | 1 42 | 1 28 |

Constant Reactance.

| | <u>1</u> | <u>7</u> | <u>12</u> | <u>8</u> | <u>10</u> |
|-----|----------|----------|-----------|----------|-----------|
| 20 | 2 34 | 3 12 | 2 47 | 3 01 | 3 57 |
| 40 | 2 20 | 2 28 | 2 15 | 2 24 | 2 39 |
| 60 | 2 16 | 2 18 | 2 04 | 2 11 | 2 14 |
| 80 | 2 11 | 2 11 | 1 59 | 2 07 | 2 04 |
| 100 | 2 07 | 2 06 | 1 58 | 2 04 | 1 59 |

Errors for 80% Power Factor.

| | Constant R. | | Variable L. | | | |
|----------|--------------|--------------|--------------|--------------|--------------|--------------|
| <u>L</u> | <u>.0050</u> | <u>.0075</u> | <u>.0100</u> | <u>.0150</u> | <u>.0175</u> | <u>.0200</u> |
| | | 20 | Amperes. | | | |
| Ratio | 1.25 | 4.80 | 8.15 | 6.80 | 5.40 | 4.50 |
| Alpha | 4.20 | 4.20 | 3.70 | 3.20 | 3.00 | 2.80 |
| Total | 5.45 | 9.00 | 11.85 | 9.80 | 8.40 | 7.30 |
| | | 40 | Amperes. | | | |
| Ratio | -0.90 | -0.50 | 2.60 | 2.65 | 1.60 | -1.50 |
| Alpha | 3.10 | 3.00 | 2.70 | 2.50 | 2.40 | 2.00 |
| Total | 2.10 | 2.50 | 5.30 | 5.15 | 4.00 | 0.50 |
| | | 60 | Amperes. | | | |
| Ratio | -1.40 | -0.85 | 0.00 | 0.25 | -0.25 | -1.75 |
| Alpha | 2.80 | 2.70 | 2.50 | 2.40 | 2.30 | 2.00 |
| Total | 1.40 | 1.85 | 2.50 | 2.65 | 2.05 | 0.25 |
| | | 80 | Amperes. | | | |
| Ratio | -2.90 | -2.65 | -1.90 | -1.60 | -1.60 | -1.75 |
| Alpha | 2.60 | 2.50 | 2.40 | 2.30 | 2.30 | 2.00 |
| Total | -0.30 | -0.15 | 0.50 | 0.70 | 0.70 | 0.25 |
| | | 100 | Amperes. | | | |
| Ratio | -3.40 | -3.60 | -2.95 | -2.85 | -2.95 | -3.45 |
| Alpha | +0.90 | 2.50 | 2.40 | 2.30 | 2.30 | 2.00 |
| Total | -0.90 | -1.10 | -0.55 | -0.55 | -0.65 | -1.45 |
| | Constant L. | | Variable R. | | | |
| <u>R</u> | <u>0.09</u> | <u>0.12</u> | <u>0.16</u> | <u>0.20</u> | <u>.024</u> | |
| Ratio | 5.65 | 1.50 | -0.50 | 0.50 | 3.15 | |
| Alpha | 3.50 | 4.30 | 4.20 | 4.80 | 4.50 | |
| Total | 9.15 | 5.80 | 3.70 | 5.30 | 7.70 | |
| | | 40 | Amperes | | | |
| Ratio | 4.00 | -1.25 | -2.35 | -1.75 | 0.50 | |
| Alpha | 3.20 | 3.30 | 3.20 | 3.00 | 3.30 | |
| Total | 7.20 | 2.05 | 0.85 | 1.25 | 2.80 | |
| | | 60 | Amperes. | | | |
| Ratio | 0.75 | -2.25 | -3.50 | -3.35 | -1.75 | |
| Alpha | 3.00 | 3.20 | 2.80 | 2.70 | 2.90 | |
| Total | 3.75 | 0.95 | 0.70 | -0.65 | 1.25 | |
| | | 80 | Amperes. | | | |
| Ratio | -0.50 | -3.10 | -4.25 | -3.95 | -2.50 | |
| Alpha | +2.90 | 3.00 | 2.70 | 2.60 | 2.80 | |
| Total | 2.40 | -0.10 | -1.55 | -1.35 | 0.30 | |

Data for Calibration Curves.

Hot Wire with
Shunt.

Hot Wire no
Shunt.

Hot Wire
Against I_2

| I_{sh} | I_{HW} | I_{sh} | I_{HW} | I_2 | I_{HW} |
|----------|----------|----------|----------|-------|----------|
| 13.2 | 10.0 | 0.32 | 10.0 | 0.75 | 0.70 |
| 23.0 | 20.0 | 0.65 | 20.0 | 1.25 | 1.25 |
| 31.0 | 30.0 | 0.92 | 30.0 | 1.655 | 1.705 |
| 41.5 | 40.0 | 1.25 | 40.0 | 2.00 | 2.005 |
| 51.0 | 50.0 | 1.54 | 50.0 | 2.415 | 2.43 |
| 61.255 | 60.0 | 1.85 | 60.0 | 2.97 | 2.98 |
| 71.5 | 70.0 | 2.15 | 70.0 | | |
| 81.75 | 80.0 | 2.43 | 80.0 | | |
| 92.0 | 90.0 | 2.71 | 90.0 | | |
| 102.0 | 100.0 | 2.98 | 100.0 | | |

Hot Wire as
Voltmeter.

Calibration
of E_m .

Voltmeter
4403.

| I_{sh} | E_m | E_{sh} | E_m | E_{sh} | E |
|----------|-------|----------|-------|----------|-------|
| 14.3 | .037 | .030 | .032 | 0.30 | 0.31 |
| 23.2 | .061 | .060 | .063 | 0.40 | 0.41 |
| 35.0 | .093 | .100 | .105 | 0.60 | 0.61 |
| 41.6 | .111 | .130 | .132 | 0.80 | 0.82 |
| 56.8 | .150 | .160 | .165 | 1.00 | 1.015 |
| 69.5 | .184 | .200 | .208 | 1.50 | 1.515 |
| 78.2 | .215 | .230 | .235 | 2.00 | 2.065 |
| 93.0 | .255 | .260 | .267 | | |
| 101.0 | .280 | .300 | .308 | | |

Dynamometer against
 I_2 and I_{ph}

Dynam. as
Ammeter.

Ammeter
106.

| D. | I_2 | I_{ph} | D | I_{sh} | I_{sh} | I |
|-------|-------|----------|-------|----------|----------|------|
| 13.5 | 2.915 | 2.90 | 5.50 | 2.00 | 1.00 | 1.00 |
| 15.0 | 3.150 | 3.15 | 7.00 | 2.25 | 2.00 | 2.03 |
| 17.0 | 3.340 | 3.34 | 10.20 | 2.75 | 3.00 | 3.06 |
| 20.0 | 3.630 | 3.62 | 12.35 | 3.00 | 4.00 | 4.10 |
| 21.8 | 3.860 | 3.84 | 14.50 | 3.25 | 4.86 | 5.00 |
| 24.0 | 4.050 | 4.05 | 16.85 | 3.50 | | |
| 27.0 | 4.230 | 4.22 | 19.70 | 3.75 | | |
| 29.0 | 4.490 | 4.49 | 22.20 | 4.00 | | |
| 31.30 | 4.700 | 4.69 | 25.60 | 4.25 | | |
| 33.5 | 4.850 | 4.84 | 28.50 | 4.50 | | |
| | | | 32.00 | 4.75 | | |
| | | | 35.25 | 5.00 | | |

Ratio Readings for Transformer #2.

25 Ampere Shunt used.

| #1. | | #3. | | #4. | | #10. | | #11. | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| I _H | I _L | I _H | I _L | I _H | I _L | I _H | I _L | I _H | I _L |
| 3.0 | 0.70 | 2.5 | 0.65 | 2 2.5 | 0.56 | 3.0 | 0.74 | 2.5 | 0.61 |
| 5.0 | 1.17 | 6.5 | 1.44 | 5.0 | 1.13 | 5.0 | 1.16 | 5.0 | 1.12 |
| 10.0 | 2.13 | 10.0 | 2.12 | 10.0 | 2.09 | 10.0 | 2.13 | 10.0 | 2.09 |
| 12.5 | 2.62 | 12.5 | 2.59 | 12.5 | 2.58 | 12.5 | 2.62 | 12.5 | 2.59 |
| 15.0 | 3.15 | 15.0 | 3.13 | 15.0 | 3.12 | 15.0 | 3.17 | 15.0 | 3.11 |
| 16.0 | 3.35 | 17.5 | 3.72 | 17.4 | 3.65 | 17.5 | 3.70 | 16.9 | 3.52 |
| 17.5 | 3.73 | 18.25 | 3.80 | | | 19.0 | 3.98 | | |
| 20.0 | 4.20 | | | | | | | | |

Data on Transformer #2.

Phase Angle.

Circuit #1.

Circuit #3.

Circuit #4.

| I_{ph} | I_L | Defl. | I_{ph} | I_L | Defl. | I_{ph} | I_L | Defl. |
|----------|-------|-------|----------|-------|-------|----------|-------|-------|
| 4.90 | 0.25 | 3.0 | 5.02 | 0.20 | 5.2 | 5.00 | 0.20 | 3.0 |
| 4.92 | 0.82 | 13.8 | 4.99 | 0.72 | 15.5 | 4.96 | 0.65 | 11.8 |
| 4.92 | 1.27 | 18.2 | 5.01 | 1.14 | 21.8 | 4.92 | 1.10 | 19.8 |
| 4.90 | 1.63 | 26.8 | 5.00 | 1.43 | 24.3 | 4.92 | 1.40 | 25.0 |
| 4.91 | 1.92 | 30.5 | 4.90 | 1.71 | 24.5 | 4.93 | 1.70 | 32.8 |
| 4.92 | 2.17 | 32.8 | 5.02 | 2.05 | 30.8 | 4.95 | 2.05 | 35.5 |
| 4.90 | 2.38 | 32.0 | 4.95 | 2.30 | 34.2 | 4.92 | 2.35 | 40.2 |
| 4.89 | 2.72 | 38.4 | 4.94 | 2.60 | 38.4 | 4.85 | 2.75 | 43.5 |
| 4.88 | 3.07 | 42.3 | 4.96 | 2.95 | 43.0 | 4.88 | 3.00 | 47.0 |
| 4.88 | 3.36 | 45.5 | 4.96 | 3.20 | 46.0 | 4.86 | 3.25 | 49.8 |
| 3.88 | 3.60 | 40.0 | 4.95 | 3.48 | 50.2 | 3.86 | 3.52 | 42.8 |
| 3.90 | 3.87 | 43.8 | 3.96 | 3.75 | 44.0 | 3.85 | 3.80 | 47.0 |
| 3.87 | 4.13 | 47.8 | 3.95 | 4.00 | 47.5 | 3.80 | 3.90 | 47.7 |
| 3.90 | 4.32 | 50.0 | 3.95 | 4.13 | 48.4 | 3.75 | 4.00 | 48.5 |

Circuit #11.


Circuit #10.

| I_{ph} | I_L | Defl. | I_{ph} | I_L | Defl. |
|----------|-------|-------|----------|-------|-------|
| 4.81 | 0.20 | 6.0 | 4.90 | 0.20 | 7.0 |
| 4.85 | 0.62 | 14.5 | 4.89 | 0.75 | 15.0 |
| 4.85 | 1.02 | 18.5 | 4.90 | 1.20 | 22.5 |
| 4.86 | 1.30 | 21.5 | 5.00 | 1.55 | 26.5 |
| 4.82 | 1.54 | 23.0 | 4.90 | 1.78 | 27.5 |
| 4.85 | 1.90 | 30.8 | 4.92 | 2.22 | 34.8 |
| 4.91 | 2.25 | 32.5 | 5.00 | 2.48 | 40.0 |
| 4.95 | 2.50 | 35.8 | 4.98 | 2.80 | 43.2 |
| 4.95 | 2.75 | 39.5 | 4.98 | 3.22 | 46.5 |
| 4.90 | 3.00 | 42.0 | 4.98 | 3.51 | 50.5 |
| 4.81 | 3.30 | 45.5 | 5.00 | 3.87 | 56.0 |
| 3.94 | 3.52 | 38.5 | 5.00 | 4.00 | 59.4 |

By means of the calibration curves of the various instruments used in the test, the data was corrected, the corrected values being used as the basis of all the curves. The preliminary curves were then drawn for each circuit with the primary current as abscissas and the ratio and the angle alpha as ordinates. From these curves values were picked for additional curves, and for convenience these values were taken for every ten amperes as shown on data sheets pp.22-25.

From these values the ratio error, angle error, and total error were determined. Evidently the ratio error in percent is equal to $100(\text{apparent ratio} - \text{true ratio}) / (\text{true ratio})$, and since the true ratio is 20, the formula resolves itself into ratio error $100(\text{apparent ratio} - 20) / 20$. A study of the ratio relations between the primary and the secondary of the series transformer, and the above equation shows that necessarily positive values of error are in favor of the consumer, since more current is flowing than is measured, and hence negative values are in favor of the station.

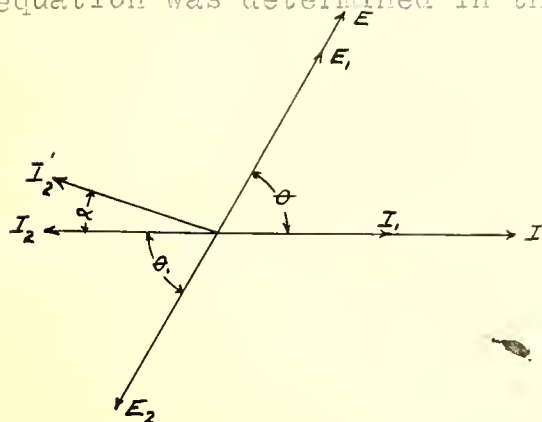The percentage angle error may be determined from the formula percent error $100(1 - \cos(\alpha + \theta)) / \cos \theta$, where alpha is the error angle as determined in preceding data, and theta is the angle of phase difference between the primary e.m.f. and current. The above equation was determined in the following manner:



Let E = E. M. F. on mains, and I = current in mains, and $\cos \theta$ = power factor. Then the power supplied = $E I \cos \theta$. In the series transformer E_1 of the primary = $K E$, and I_1 of the primary = $K I$, and $\cos \theta$ is common,



thus $E_1 I_1 \cos \theta = K E I \cos \theta$, that is, the power in the primary of the transformer is proportional to the power in the mains.

Assuming ideal transformer relations and a ratio of 1 to 1, the latter merely for convenience as any ratio will lead to the same result, the $I_2 = I_1$ and is 180 degrees out of phase with it, also $E_2 = E_1$ and is 180 degrees out of phase with it, hence, $E_2 I_2 \cos \theta = E_1 I_1 \cos \theta = K E I \cos \theta$, which states that $E_2 I_2 \cos \theta$ is a measure of the true power supplied, based on ideal conditions. Due to the resistance and the reactance of the transformer the phase angle difference in the primary and the secondary may differ by some small angle α , and hence the power registered on the secondary side would be $E_2 I_2' \cos(\theta + \alpha)$, and since $E_2 = E_1$ and $I_2' = I_1$, the power registered would be $E_1 I_1 \cos(\theta + \alpha)$. The error would then be

$$100 (E_1 I_1 \cos \theta - E_1 I_1 \cos(\theta + \alpha)) / E_1 I_1 \cos \theta = 100 (1 - \cos(\theta + \alpha)) / \cos \theta.$$

As the angle is a lag angle, the error caused thereby is always in favor of the consumer, and is therefore considered a positive error. The algebraic sum of the ratio error and the angle error gives the total error. It is this total error which is used as ordinates in curves 13-24. A study of the data for these error curves shows that the total error for 100% power factor and the ratio error differ only slightly, so that only the ratio error ^ucurve for 100% power factor was plotted.

A series of angle and ratio values were taken from the circuit curve, for 25%, 50%, 75%, 100%, and 125% of full load, grouping those results with the same resistance and variable reactance, and also those with the same reactance and variable resistance. In the first case the angle α and the ratio were plotted against the reactance, while in the latter case they were plotted against the resistance.

For points on these curves, the error was calculated and plotted against resistance and inductance. Circuit #10, the nearest approach to practical conditions, with a resistance equal to that of 100 feet of #14 B.S. wire and a low inductance, was then selected, and the total error for different power factors plotted against power factor, for different loads. A sample calculation of the above is shown in the following:

Circuit #10 on page 20 is taken as the standard because it is the nearest to actual conditions.

$$I_p = 5.00 \quad \#I_{ph} = 4.98 \quad I_s = 0.35 \quad \#I_s = 0.35 \quad \text{Defl.} = 16.0 \quad E = 81.70$$

$$\sin a = \frac{16.0}{4.98 \times 0.35 \times 81.70} = .1121 \quad a = 6^\circ 26.2'$$

From ratio readings on page 13 a curve was plotted between the primary and secondary currents. Then by taking I_p corresponding to secondary current $I_s = 0.35$, a value of $I_p = 7.5$ was obtained. This gives a ratio of $7.5/3.5 = 21.40$. These values of ratio and alpha are plotted against I_p on curve sheet #9. Points picked off of these curves for every ten amperes are tabulated on page 24.

From this data take $I_p = 20$. Then ratio is 20.98 and error is $100(20.98 - 20.00)/20$ or 4.90%. Alpha for same I_p is $3^\circ 57.0'$.

$$\% \text{Error} = 100 - 100 \cos(\theta + a) / \cos \theta. \quad \text{For an } 86.7\% \text{ power-factor}$$

$$\theta = 30^\circ \text{ and } (\theta + a) = 33^\circ 57.0'. \quad \cos 30^\circ = .867 \quad \cos 33^\circ 57' = .8295.$$

This gives an error of 4.2%. Total error is $4.9 + 4.2 = 9.1\%$. Values obtained as above are plotted against I_p on curve sheet 20.

Page 25 gives the values of ratio and alpha for the different circuits where R is constant and L is variable and also where L is constant and R is variable. These plotted against R and L give curve sheets 24 and 25. The errors for the same for 80% power-factor are tabulated on page 26 and the curves plotted from this data are on curve sheets 26 and 27.

A general consideration of the curve sheets show the following conclusions;

Ratio, Angle, - I_p Curves.

The ratio and the angle decrease with increased load as does also the error due to these.

Angle - Resistance Curves.

The angle approaches zero for zero resistance. A maximum angle occurs at .13 ohms. A minimum at .20. An increase of load straightens out the curves and tends to make the angle error constant for all resistances. It also decreases the angle.

Ratio - Resistance Curves.

Transformer circuit has a critical resistance which gives a minimum value to the ratio either a decrease or increase in the resistance raising the ratio. For any resistance an increase in load decreases the value of the ratio. Curves show that there are two resistances that will give the true value to the ratio for any load.

Angle - Inductance Curves.

The angle decreases with load. The critical value of inductance at which alpha is a maximum is .006 henrys. Any increase or decrease in the inductance decreases this angle.

Ratio - Inductance.

An increase in the inductance lowers the ratio and makes it more constant. For high loads the ratio is nearly constant for all values of L. The curves indicate a critical maximum and a minimum.

Power factor - Error.

The error decreases with an increased power factor.

Resistance - Error Curves.

The total error varies ~~directly~~ inversely as the load and may be negative. There is a critical value of R which gives a minimum error.

Inductance - Error Curves.

The total error varies inversely as the load and may be negative. A critical value of R gives a maximum error.


A consideration of the above shows that the inductance and resistance in the secondary play an important part in the correct operation of the series transformer for switch-board use. Where the instrument leads and transformer are calibrated together and used together the errors shown in the curves are eliminated. But this is not the practice as the position of the instruments may be changed or the resistance of the leads cannot be determined at the time of calibration.

That this is an important consideration is shown by the fact that the errors in some of the circuits approach very large values on light loads and values that cannot be neglected even on the usual operating loads. The average error will introduce a loss to any station sufficiently large to make it worth while for them to investigate this error.

It is customary in making a series transformer test to merely test the ratio of transformation. This of course is made on the assumption that the current and e.m.f. in the secondary of the transformer bear the same relation to each other that the current and e.m.f. in the primary do, or of not, that the error introduced thereby is negligible. That this is a serious mistake will be noted


after a study of the curves and the data.

It will be noted that at about the usual operating power factor at light loads, the error due to the phase difference of the current and e.m.f. in the secondary often exceeds that due to the ratio, while at normal operating loads it is equal to or slightly greater than the ratio error. For full loads the angle error is usually smaller than the ratio error, and for power factors of 100% or nearly so, the angle error can be neglected. Since the usual operating power factor is often much below 100%, the error due to the phase angle should also be considered in connection with that due to the ratio.

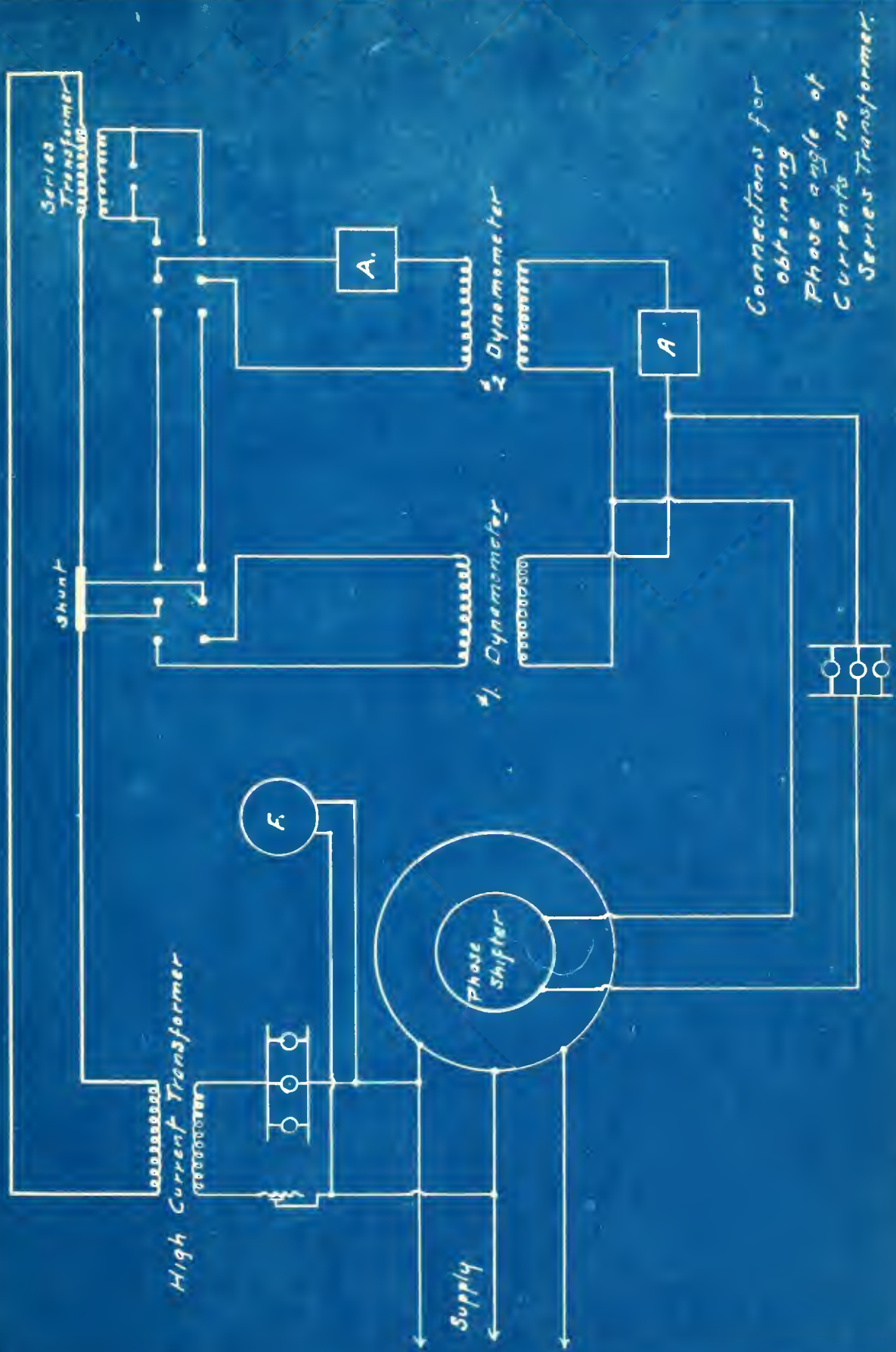


Connections for
obtaining
Phase angle of
Currents in
Series Transformer.

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY

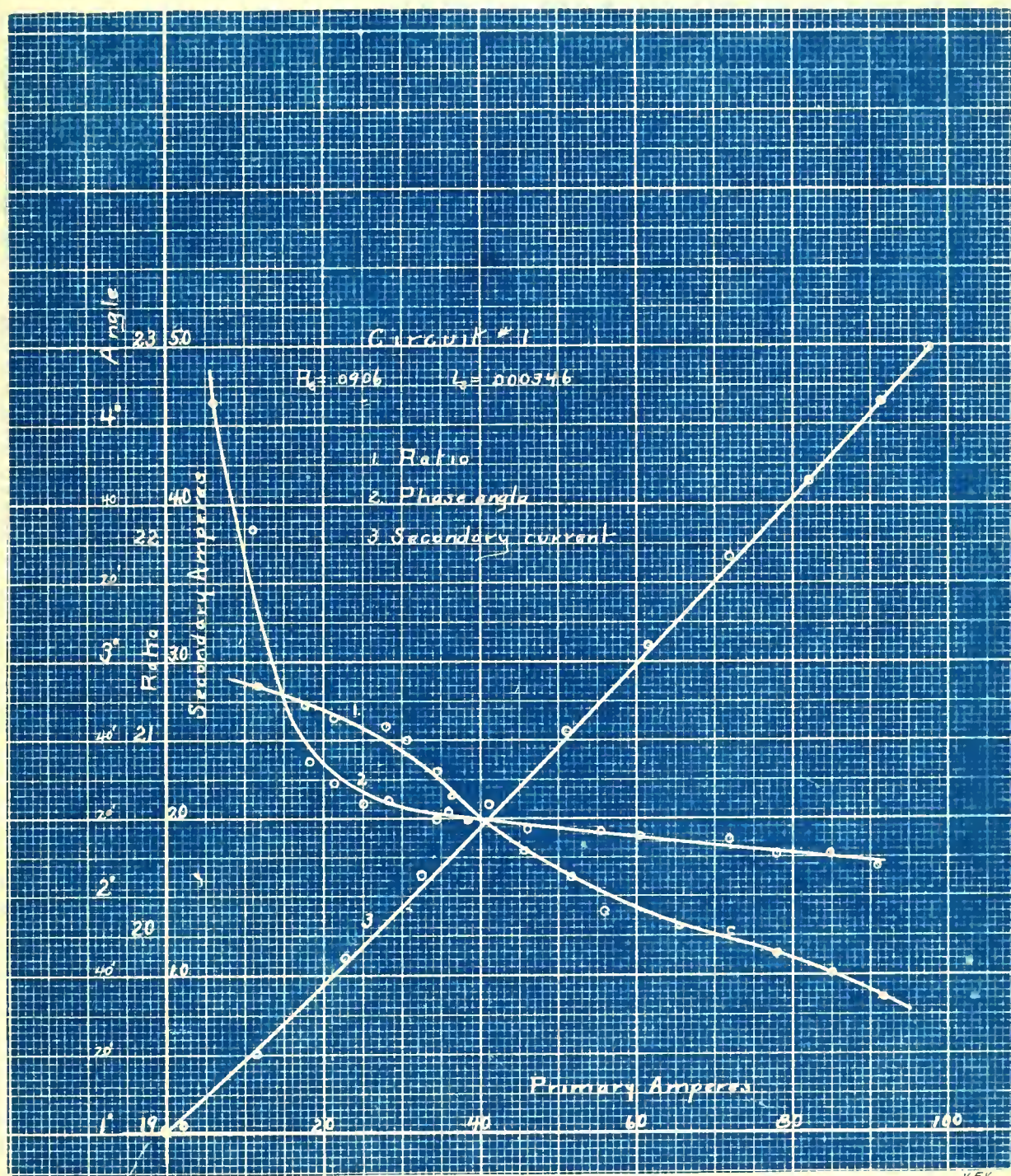

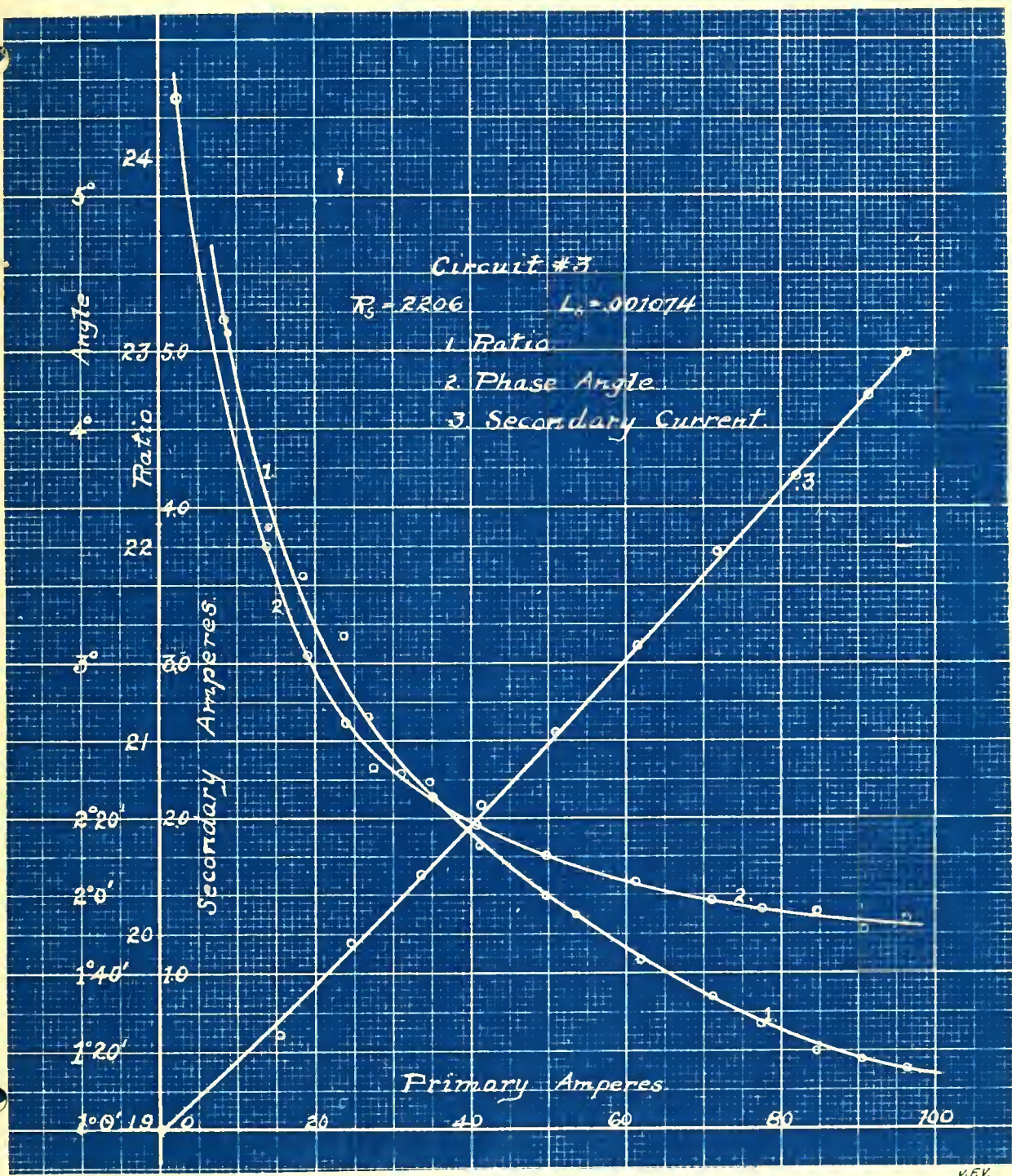
ARMOUR
INSTITUTE OF TECHNOLOGY
Chicago, Ill.




E.M.B.

V.F.V.

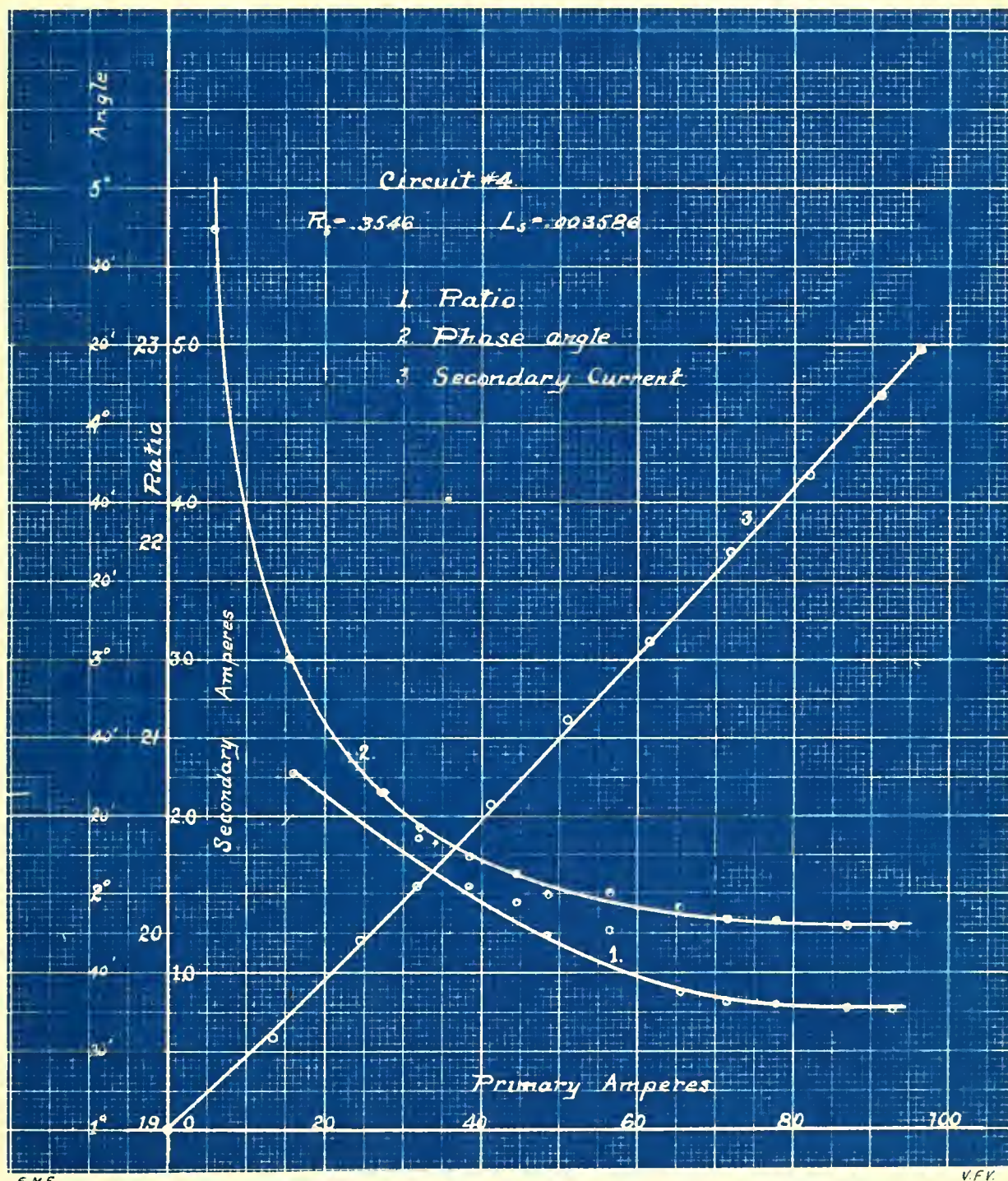ANDERSON
INSTITUTE OF TECHNOLOGY
LIBRARY,



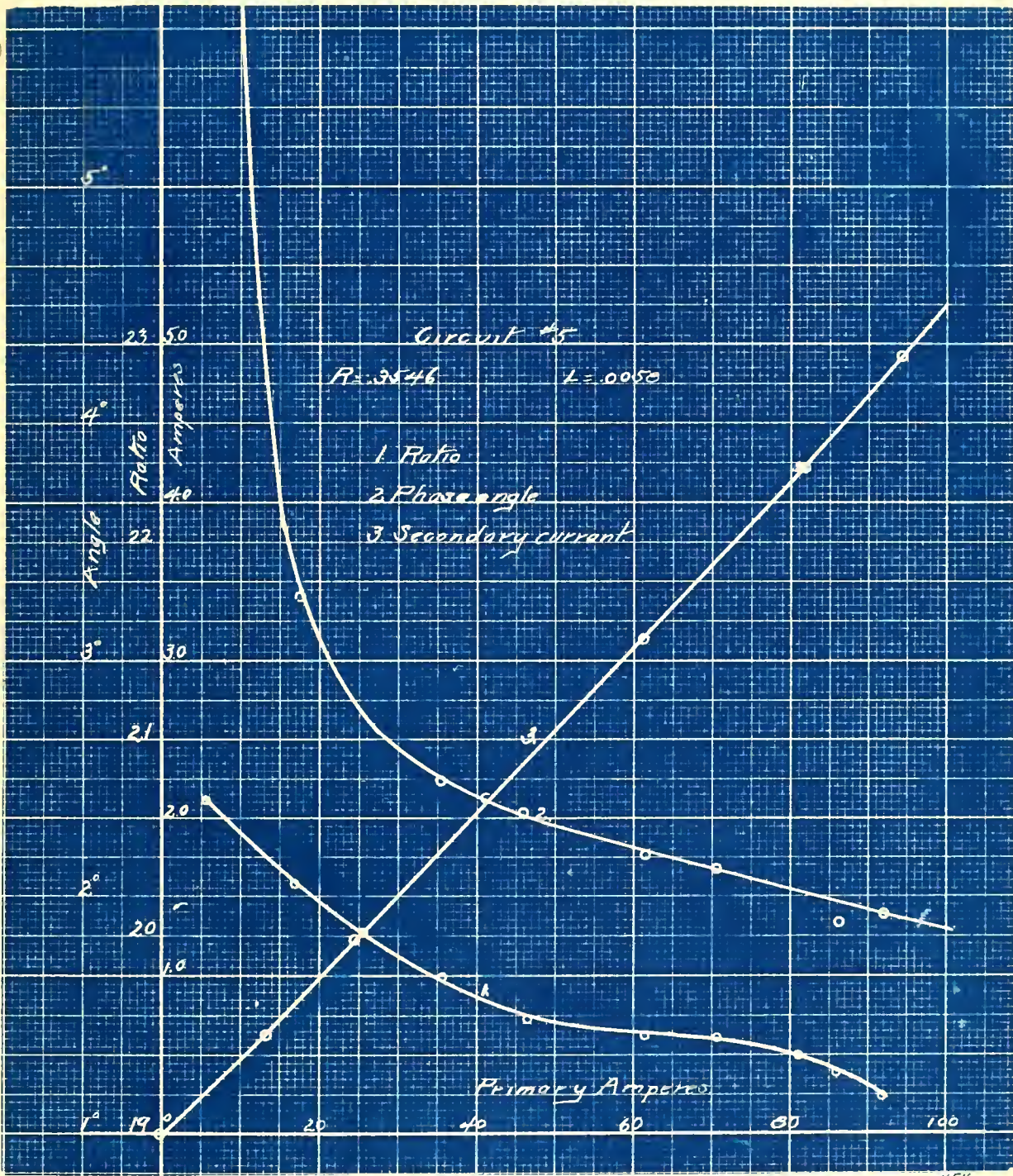
ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.



E.M.B.

V.F.V.


ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

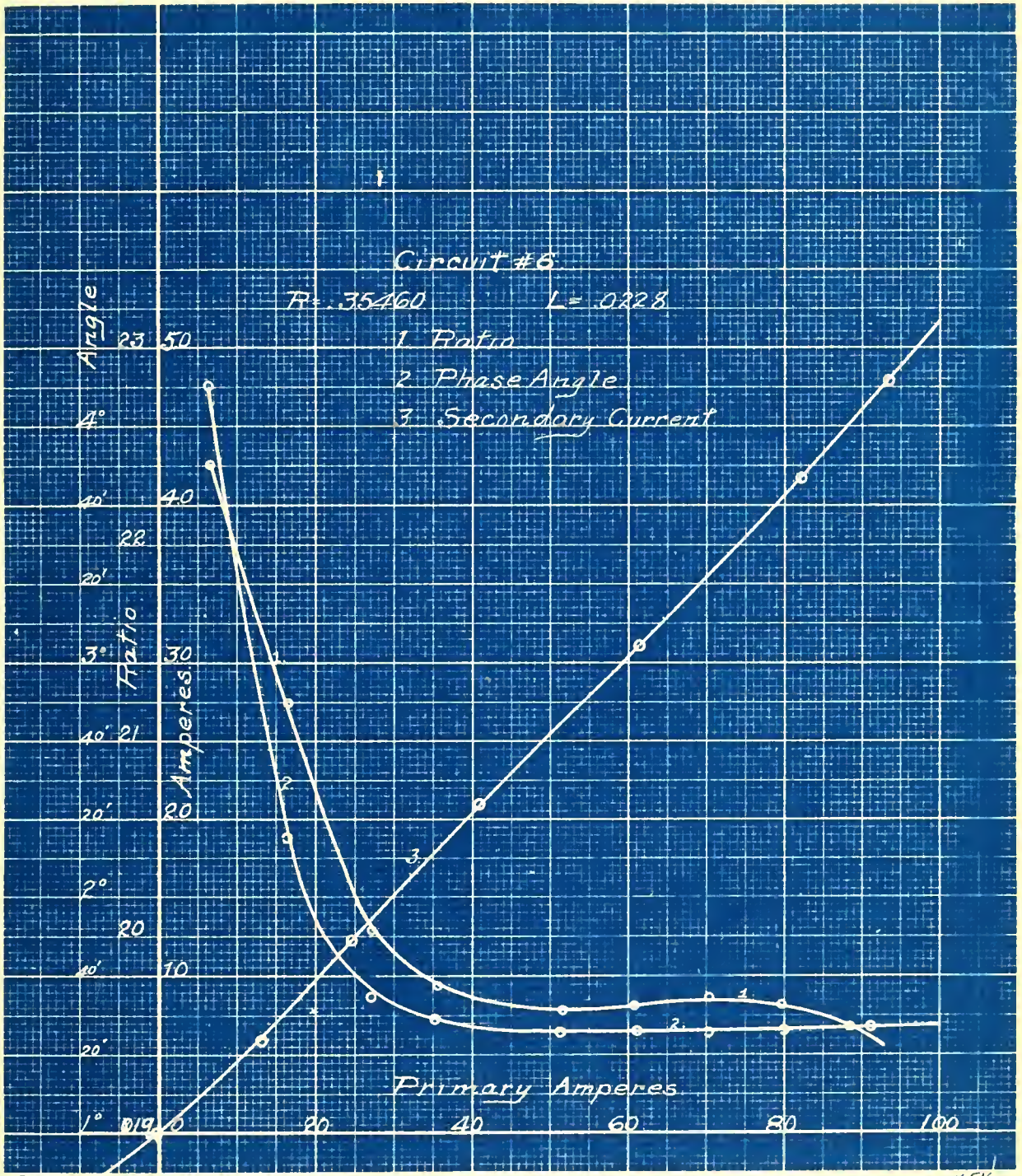

E.M.B

V.F.V.

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY,

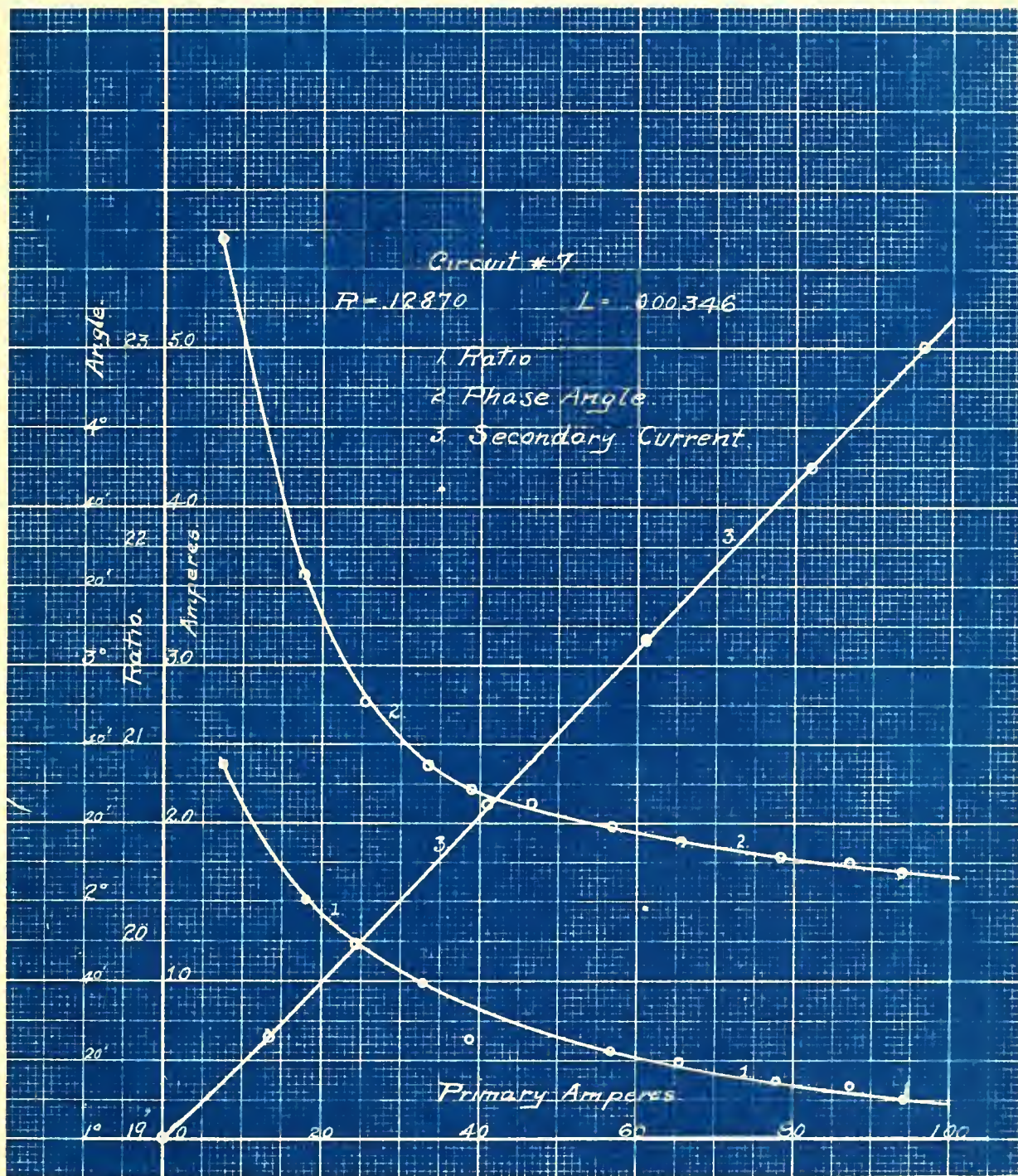

E.M.B.

V.F.F.

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

Circuit #8

$R = .2292$

$L = .0003460$

1 Ratio

2 Phase Angle

3 Secondary Current

Angle

4°

30°

20°

10°

0°

Ratio

3.0

2.0

1.0

0.5

0.2

0.1

Amperes

19

20


40

60


80

100

Primary Amperes

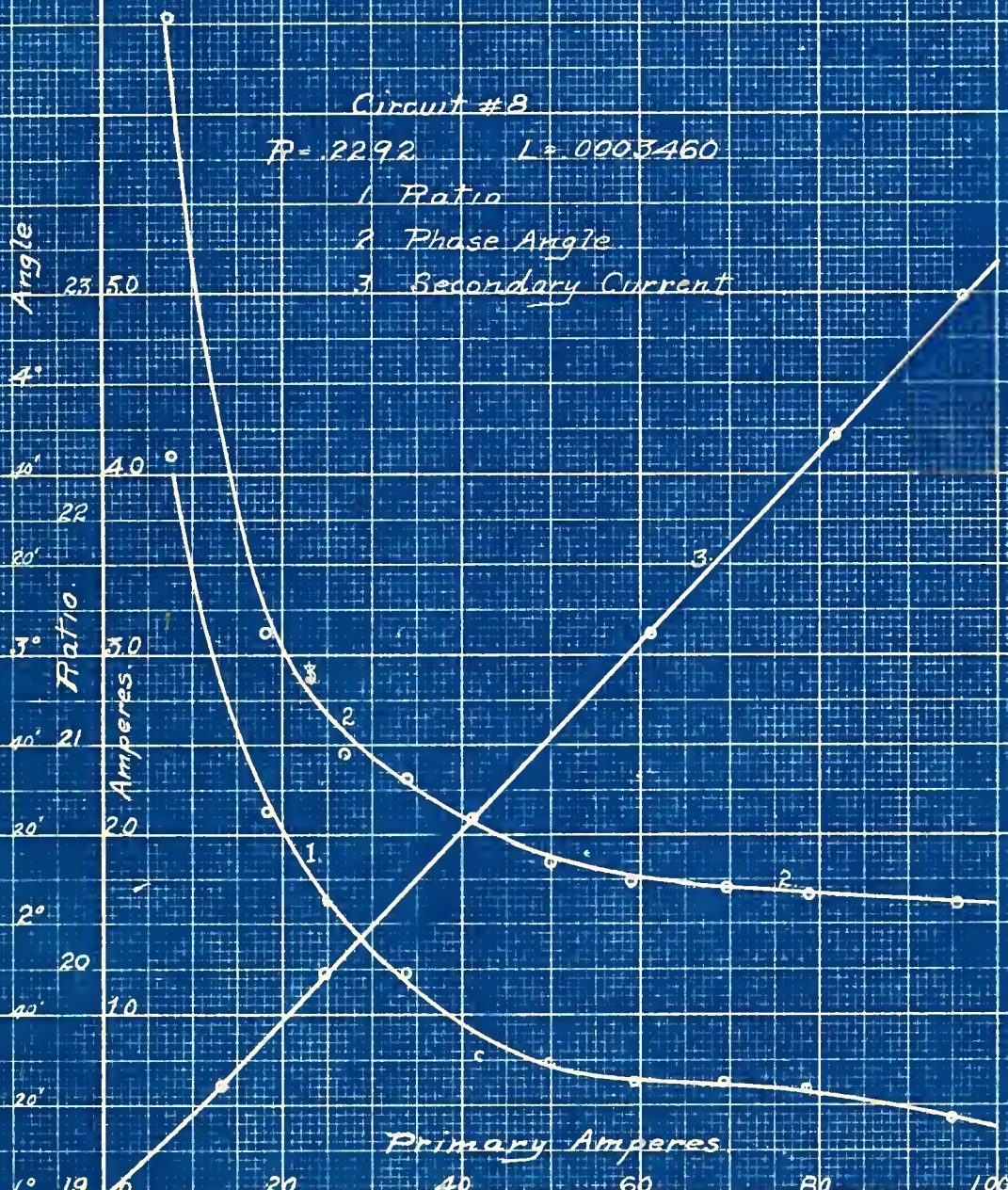


ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY,

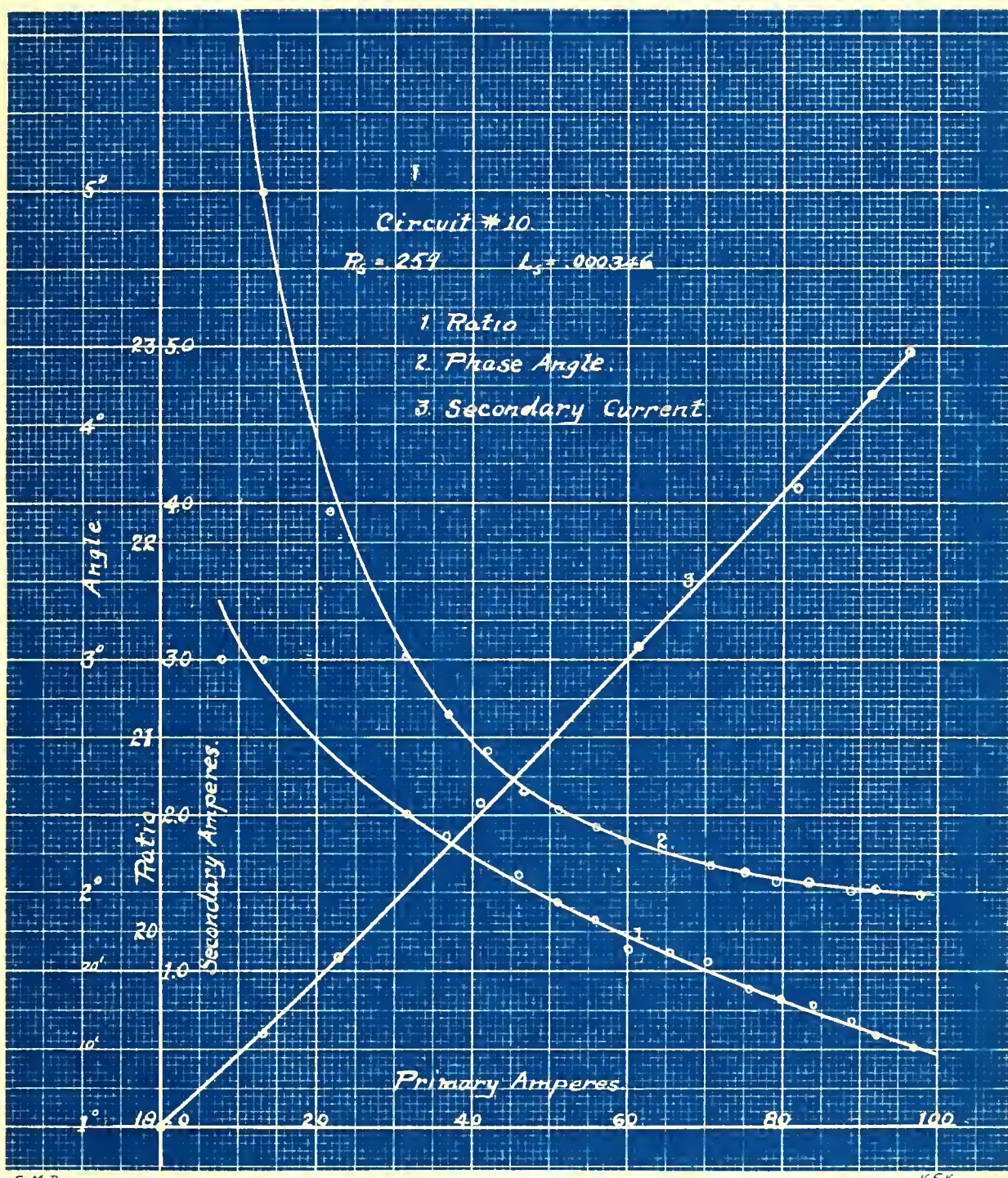

E.M.B.

V.F.F.

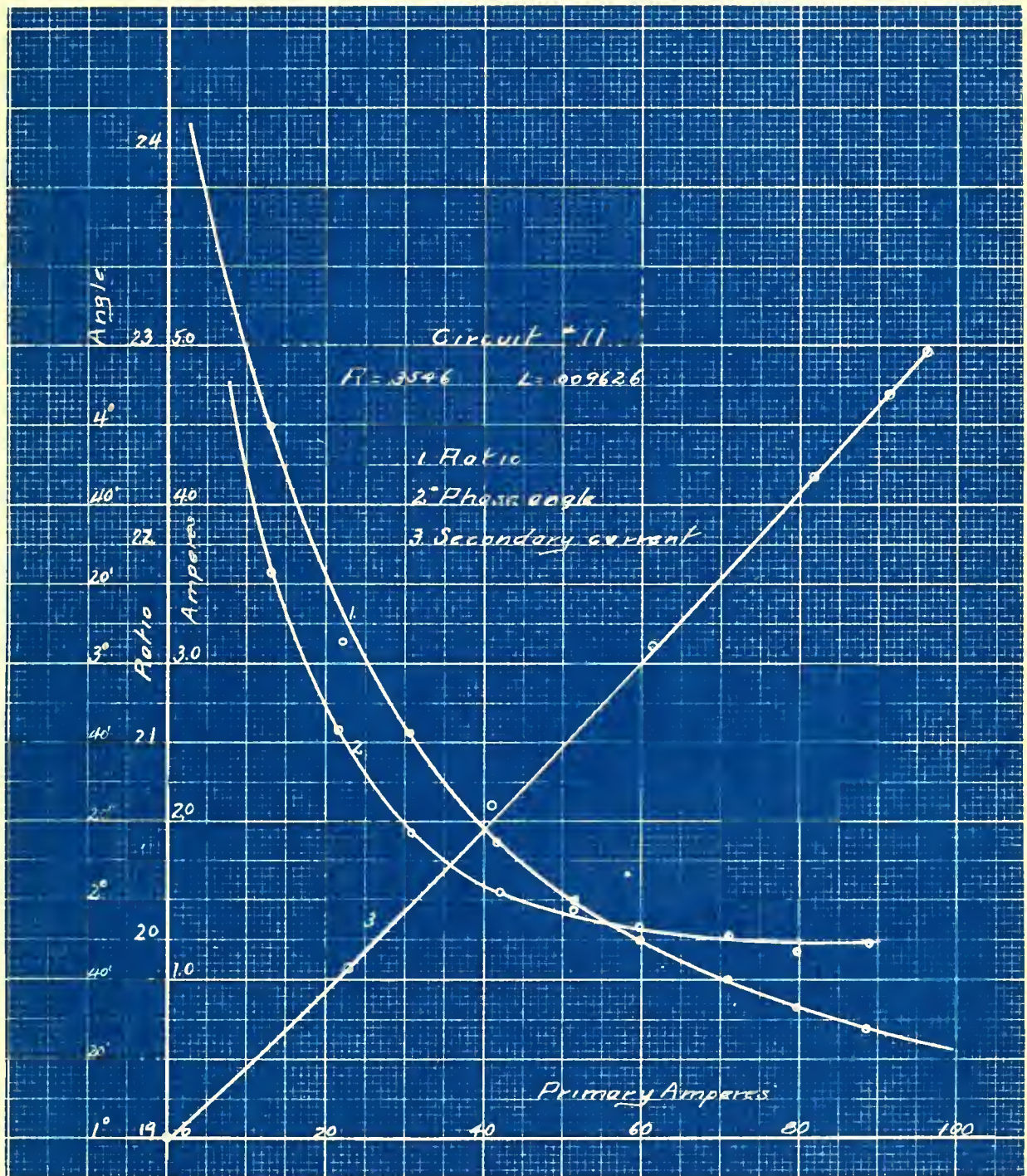ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.



ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.

Circuit #12

 $R = .212$ $L = .000346$

Angle

23 50

1 Ratio

2 Phase Angle

3 Secondary Current

40°

40

26°

22

3°

30

40°

21

20°

20

2°

20

40°

10

20°

10

1°

10

40°

10

20°

10

1°

10

40°

10

20°

10

1°

10

40°

10

20°

10

1°

10

40°

10

20°


10

1°

10

Primary Amperes

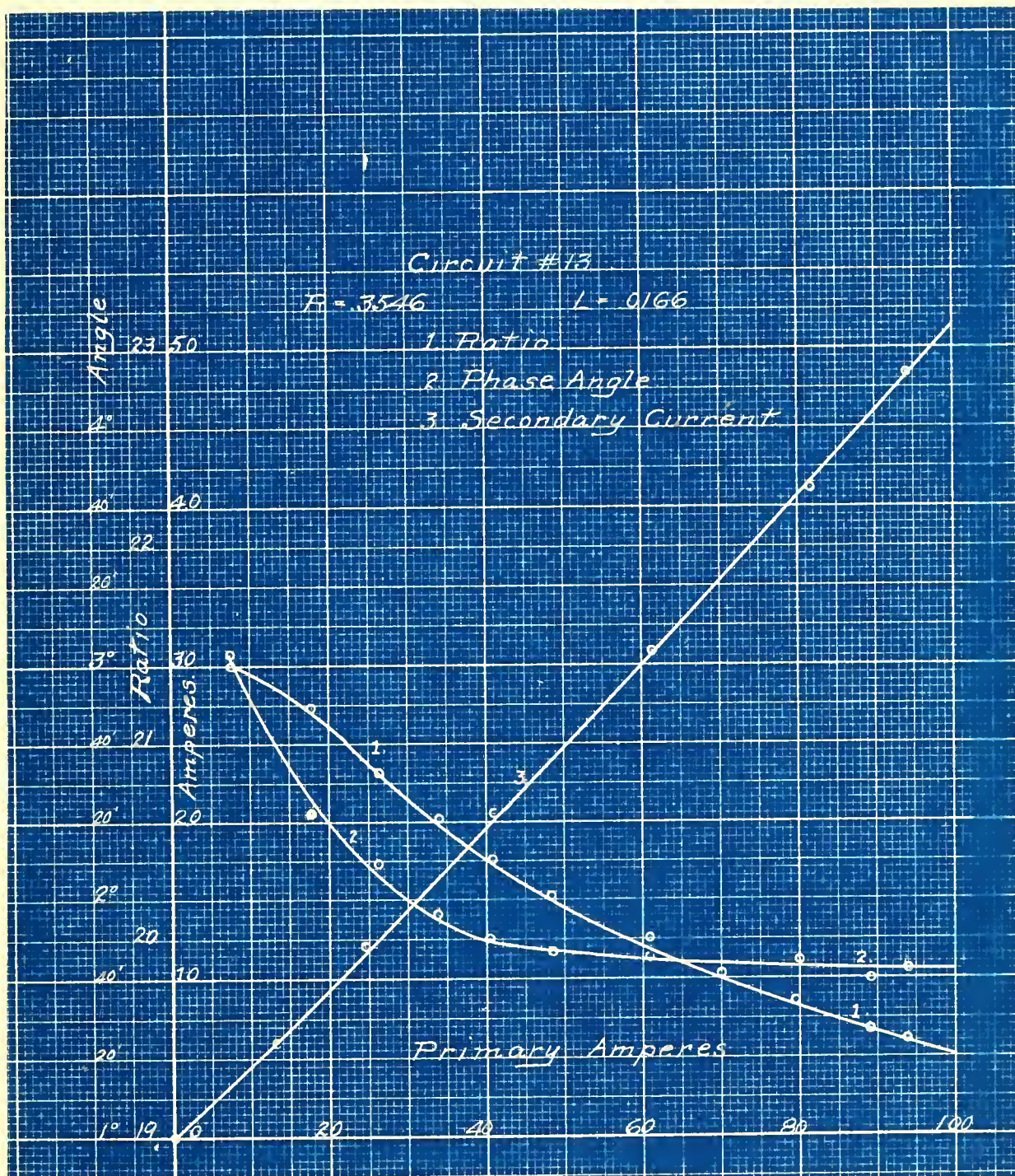
ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.




E.M.B.

V.F.V.

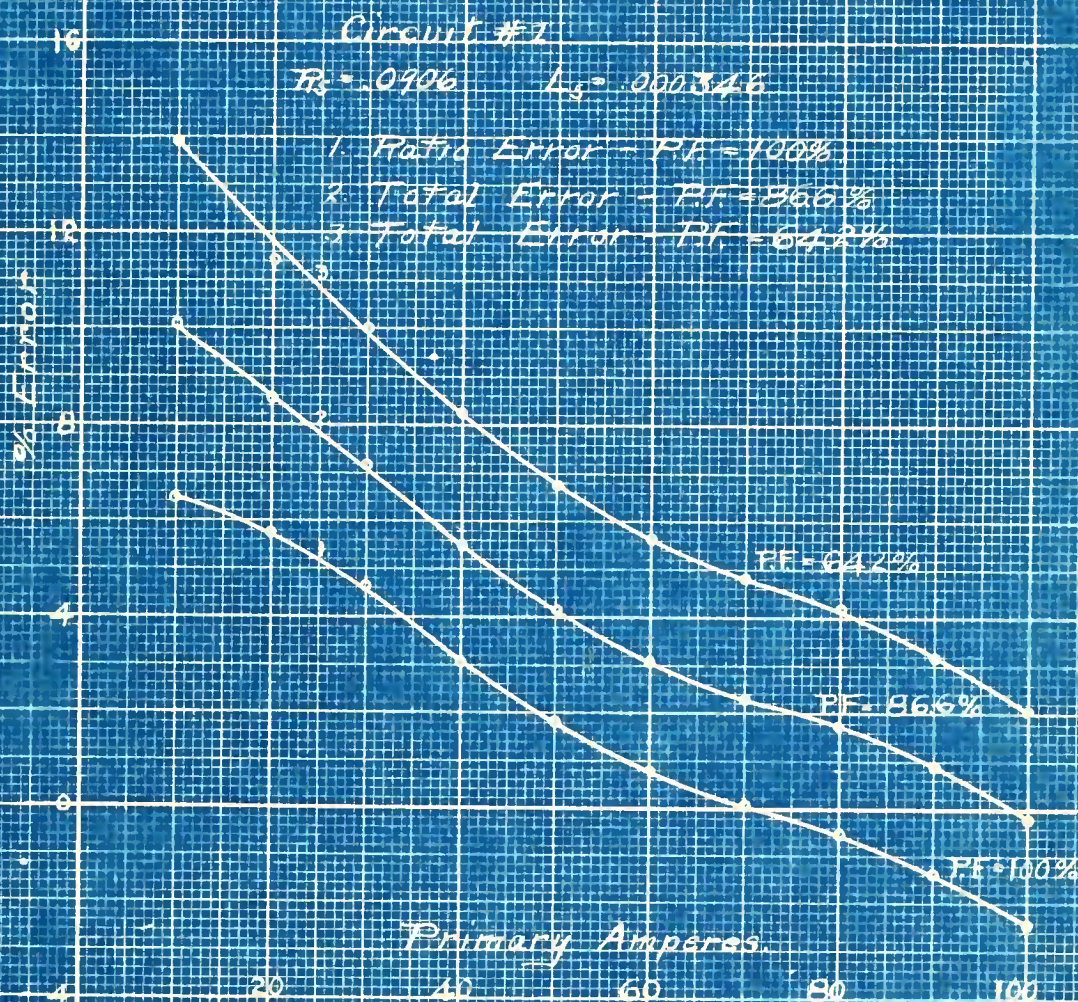ARMOUR
INSTITUTE OF TECHNOLOGY
BOSTON, MASS.



ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY,

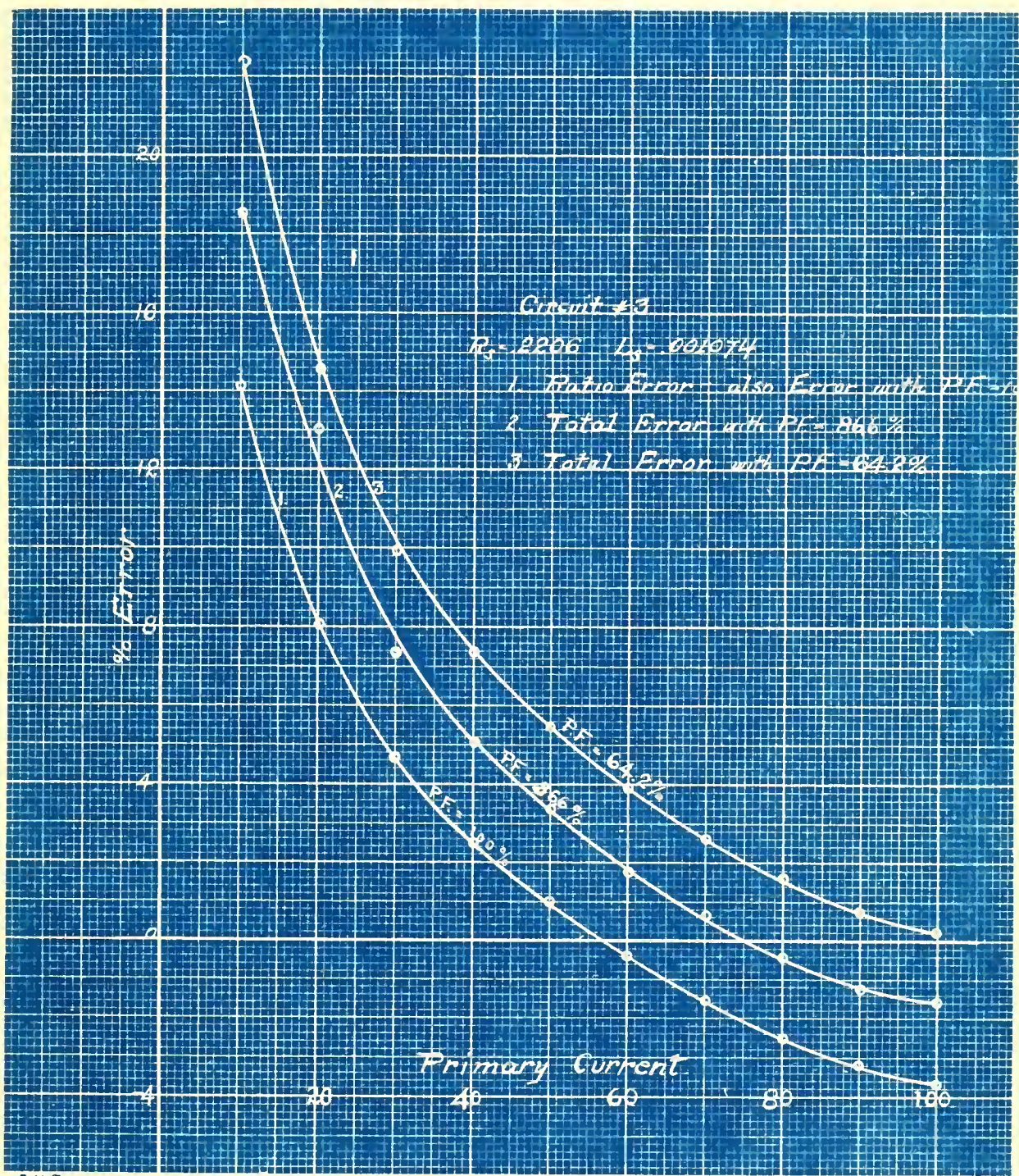

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

Circuit #4

$R_p = .75946$

$L_p = .002586$


1. Ratio Error = also Total Error with P.F. = 100%

2. Ratio Error + Phase Error P.F. = 86.6%

3. Total Error with P.F. = 64.2%

% Error

Primary Current

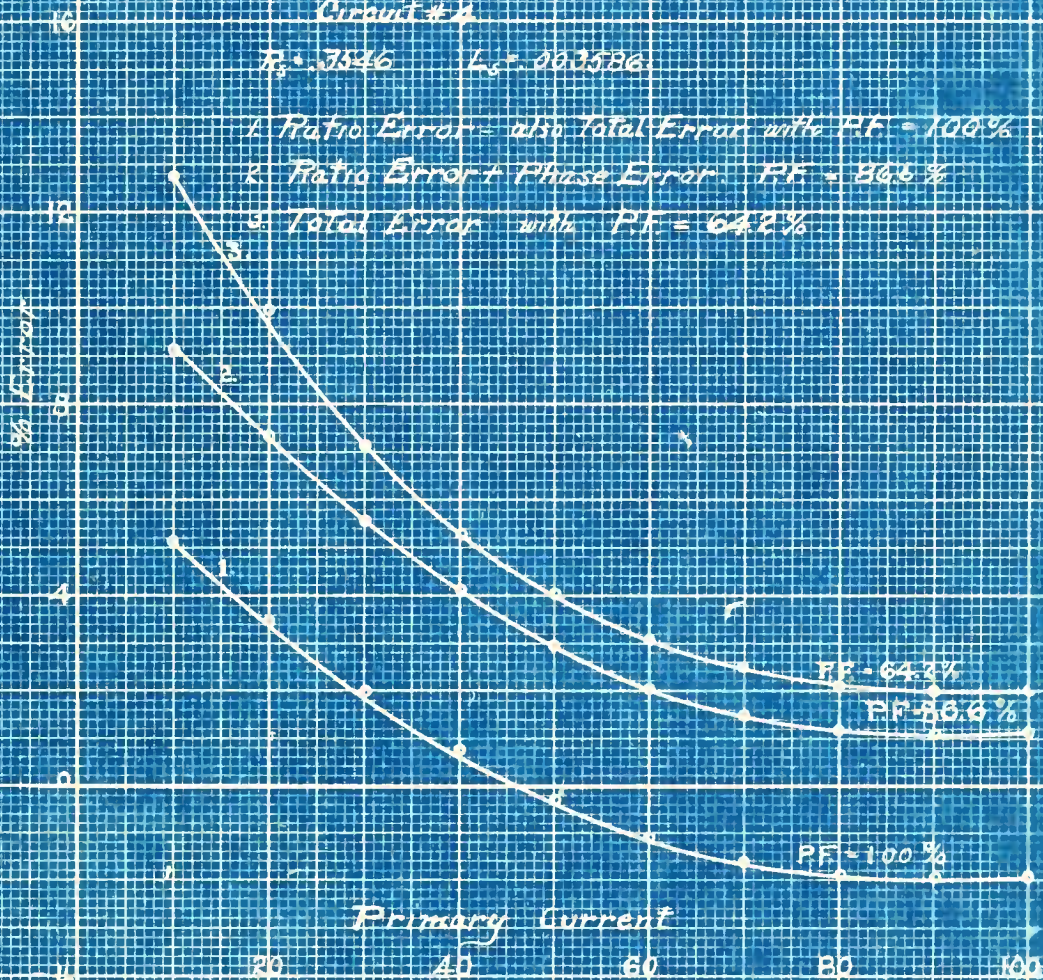

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.


Circuit #5

 $R = .3546$ $L = .0058$


1 Ratio Error - PF = 100%

2 Total Error - PF = 86.6%

3 Total Error - PF = 64.2%

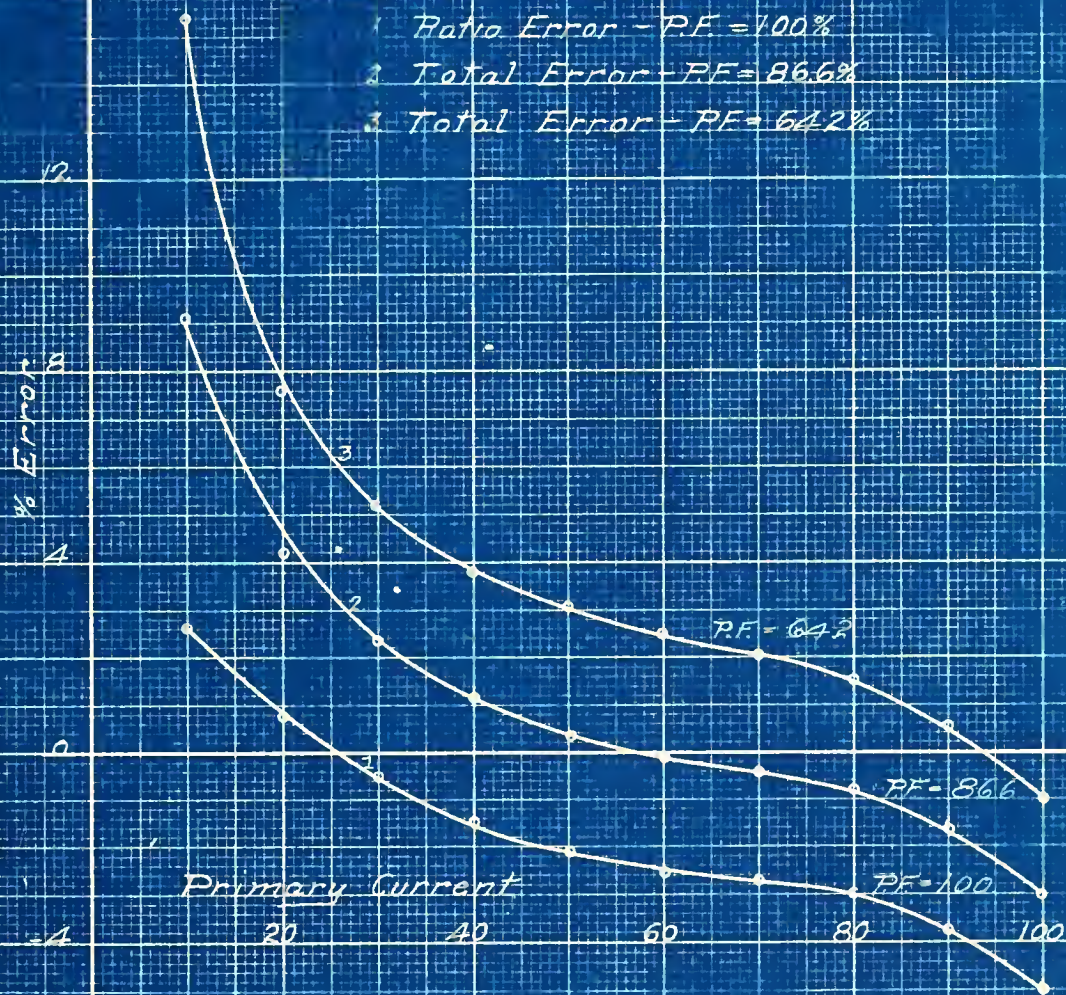


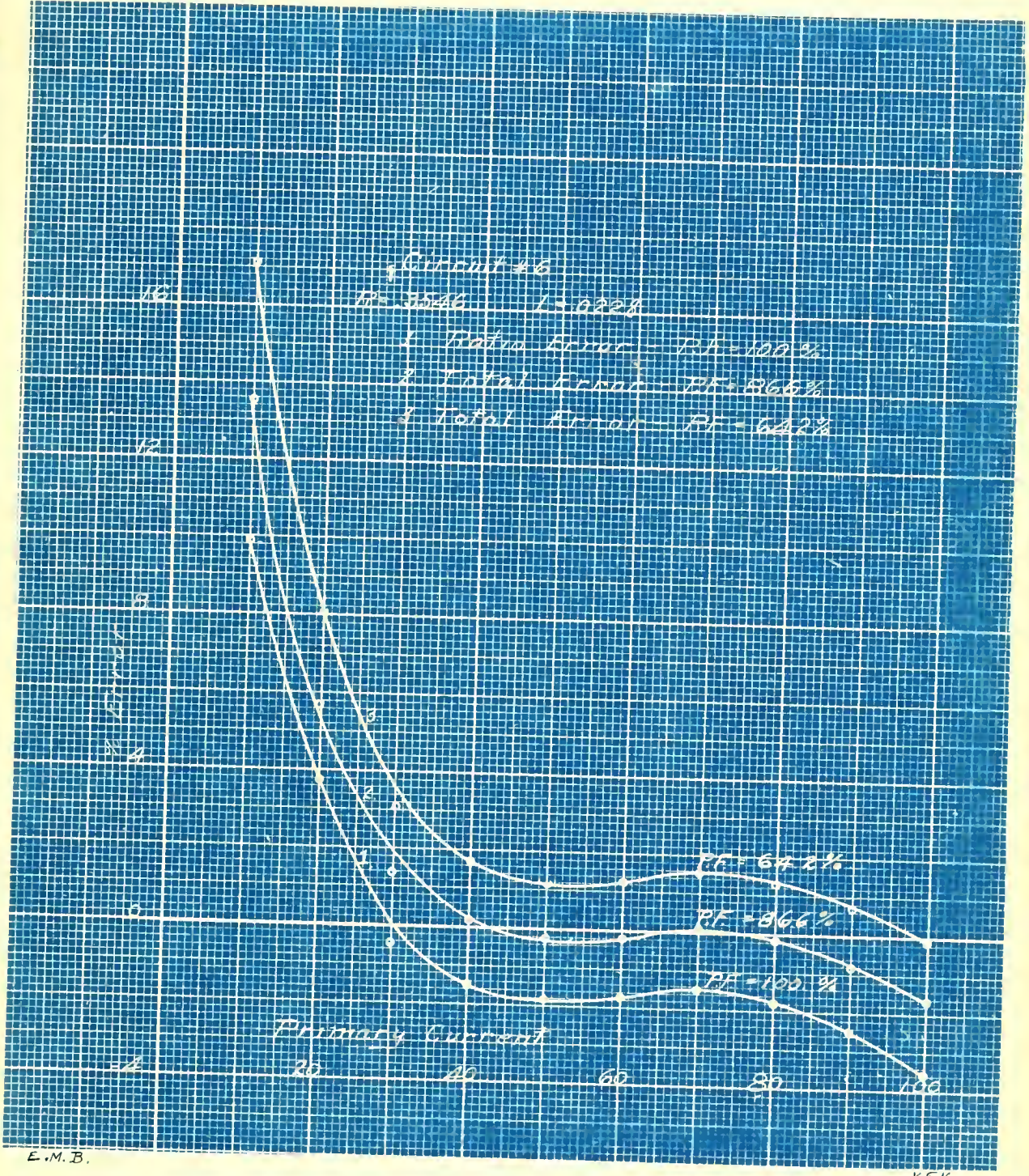ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.




ARMOUR
INSTITUTE OF TECHNOLOGY


RECEIVED

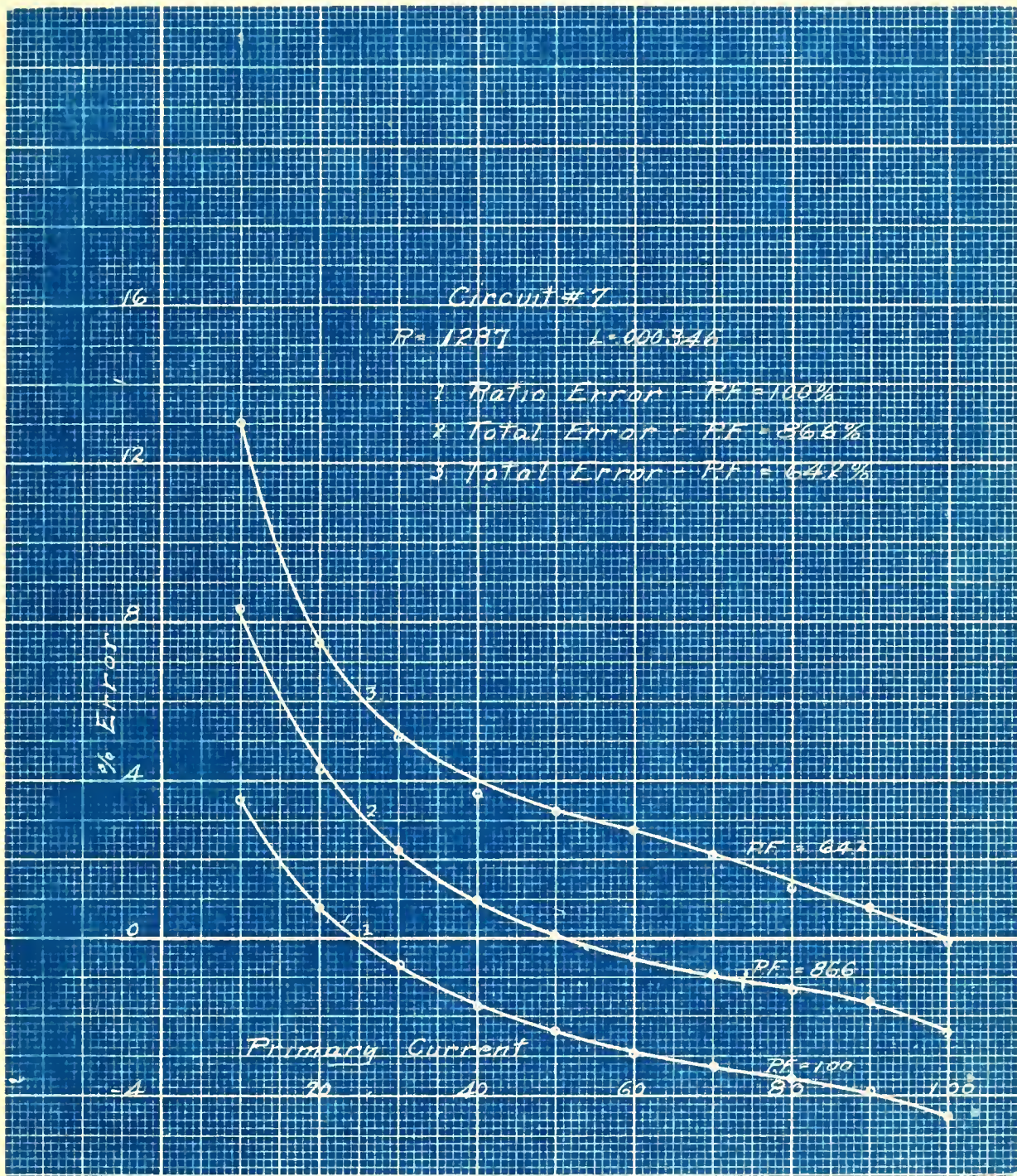


ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

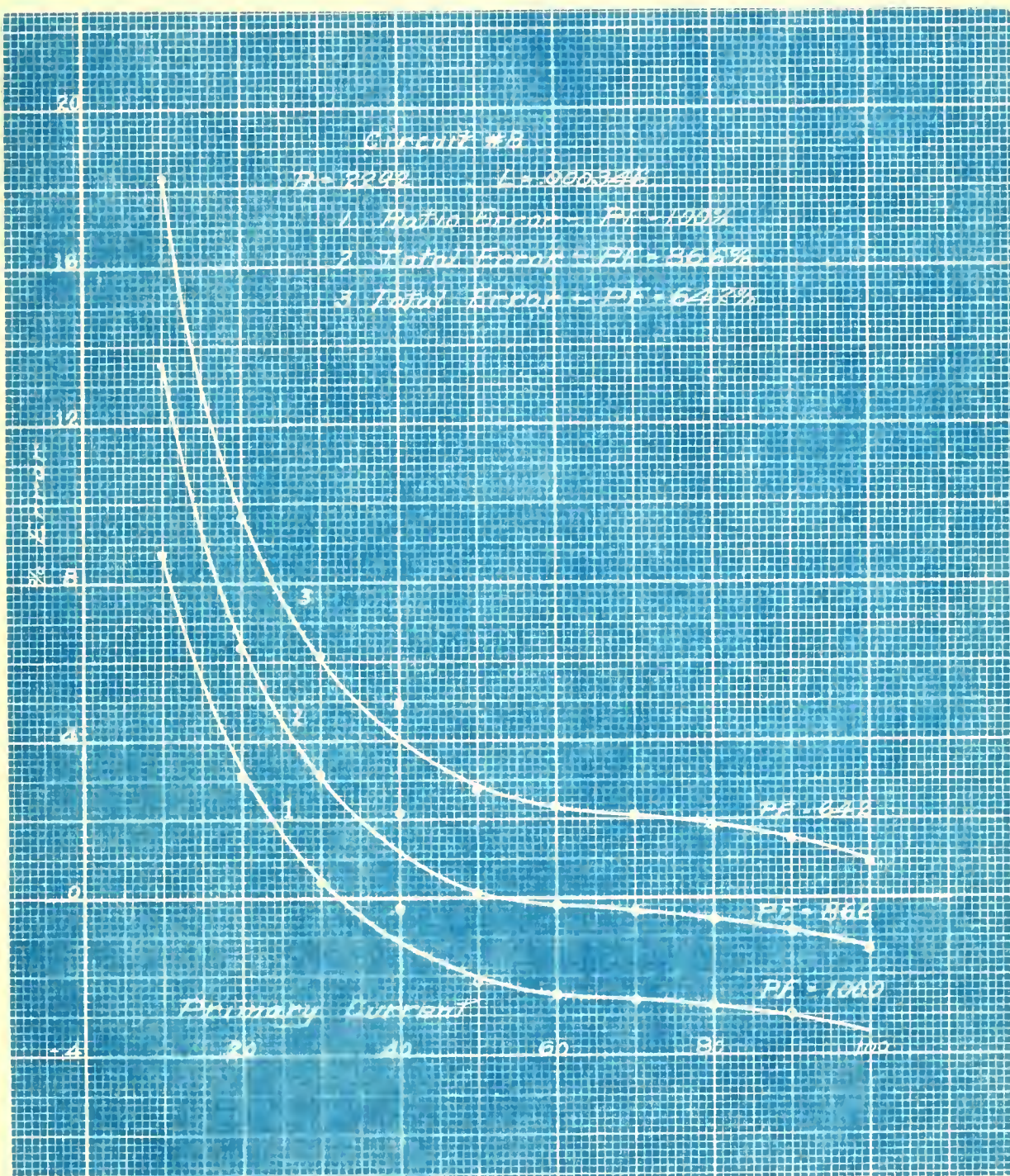


ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

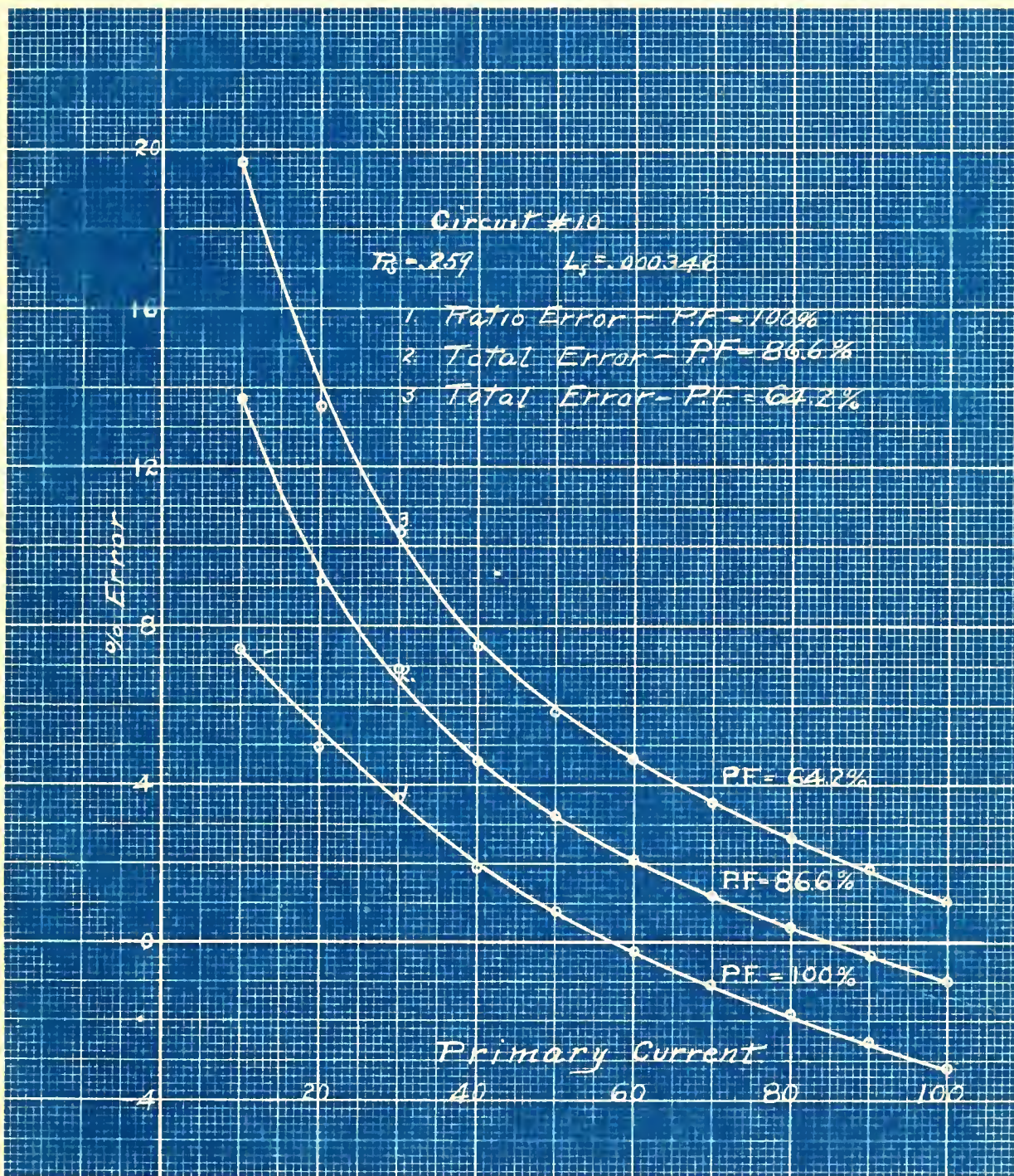

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY

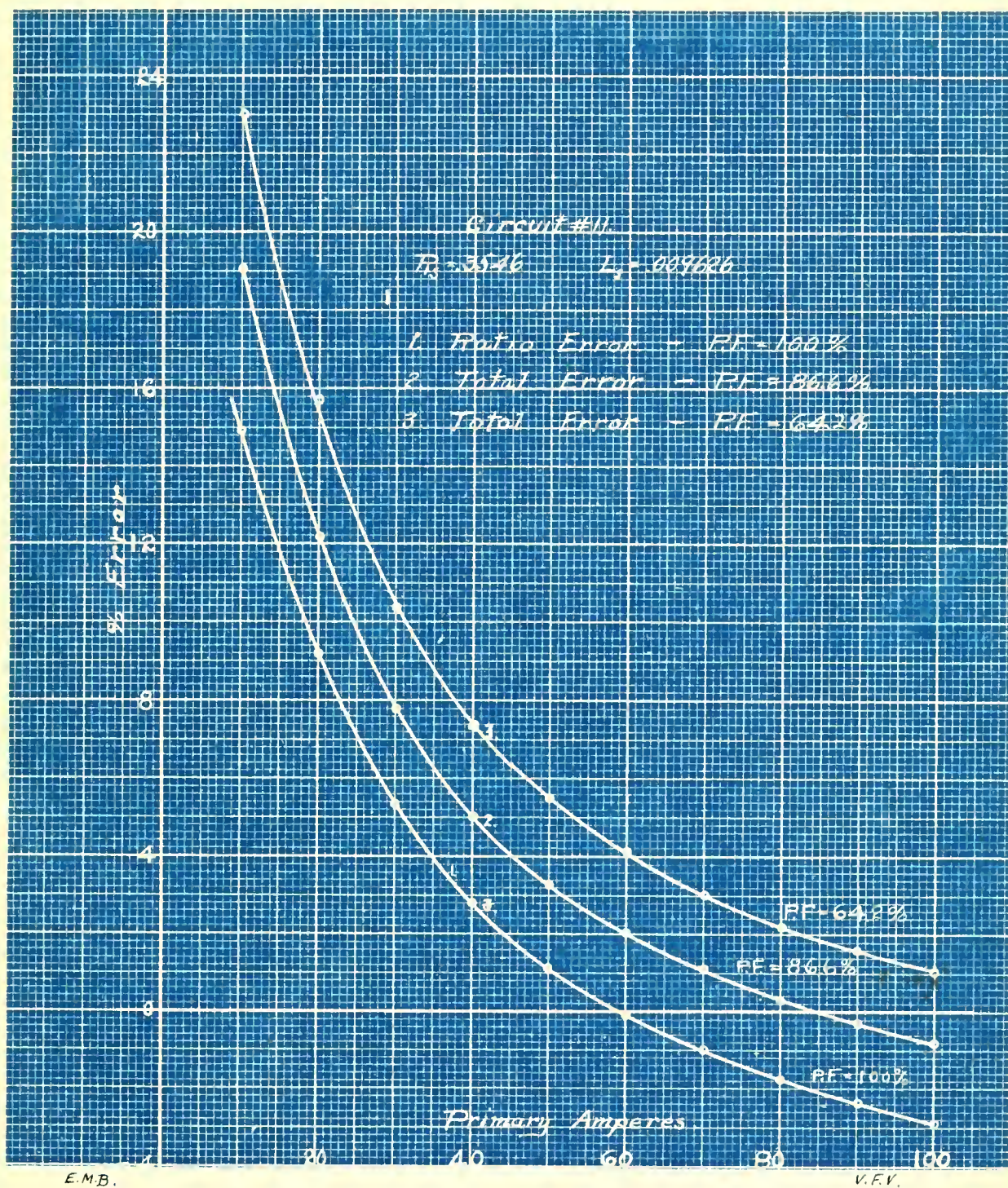

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

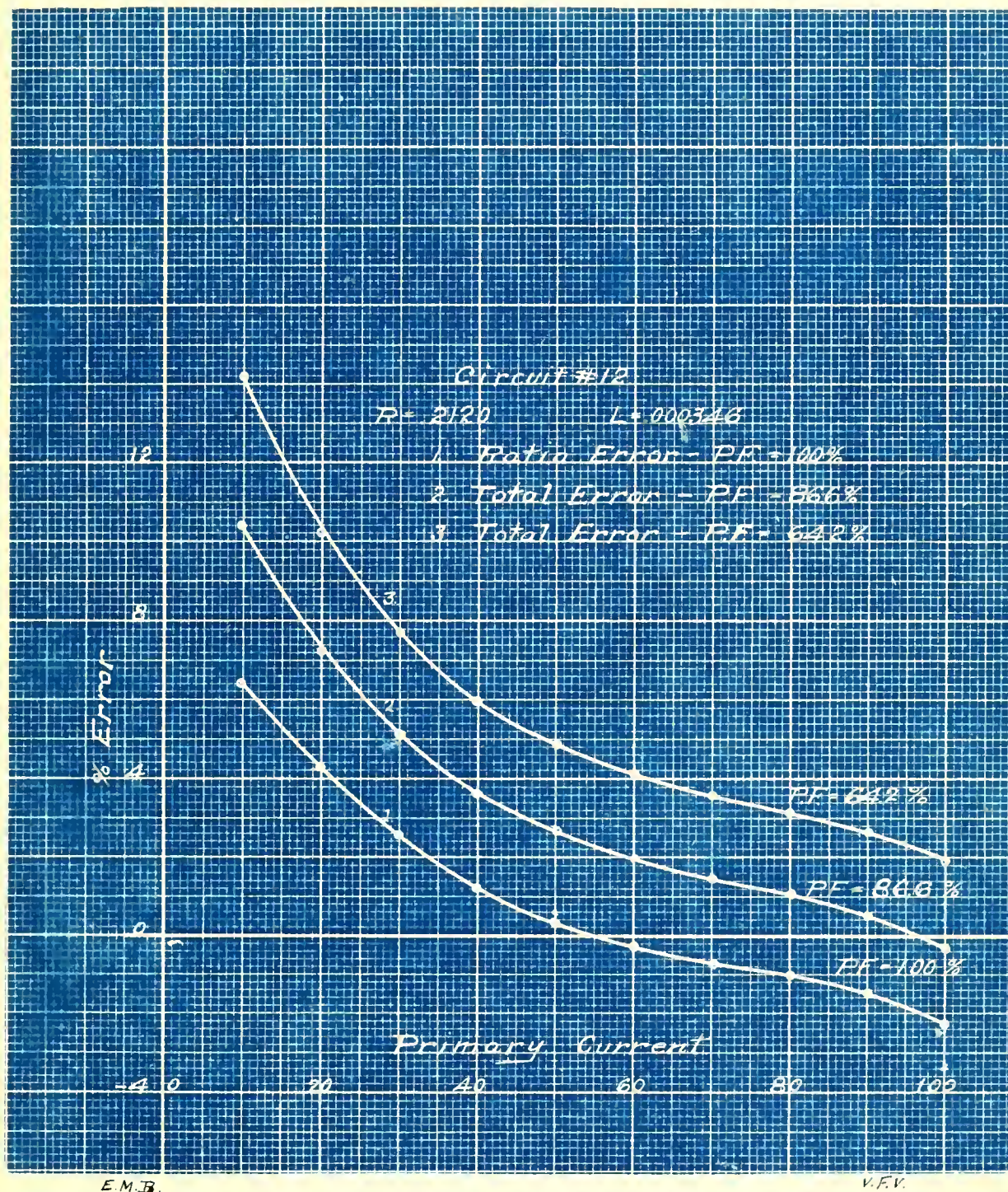

ARMOUR
INSTITUTE OF TECHNOLOGY

RECEIVED


Circuit #13

$P = .3546$ $L = .0166$

1 Ratio Error - PF = 100%

2 Total Error - PF = 86.6%


3 Total Error - PF = 64.2%

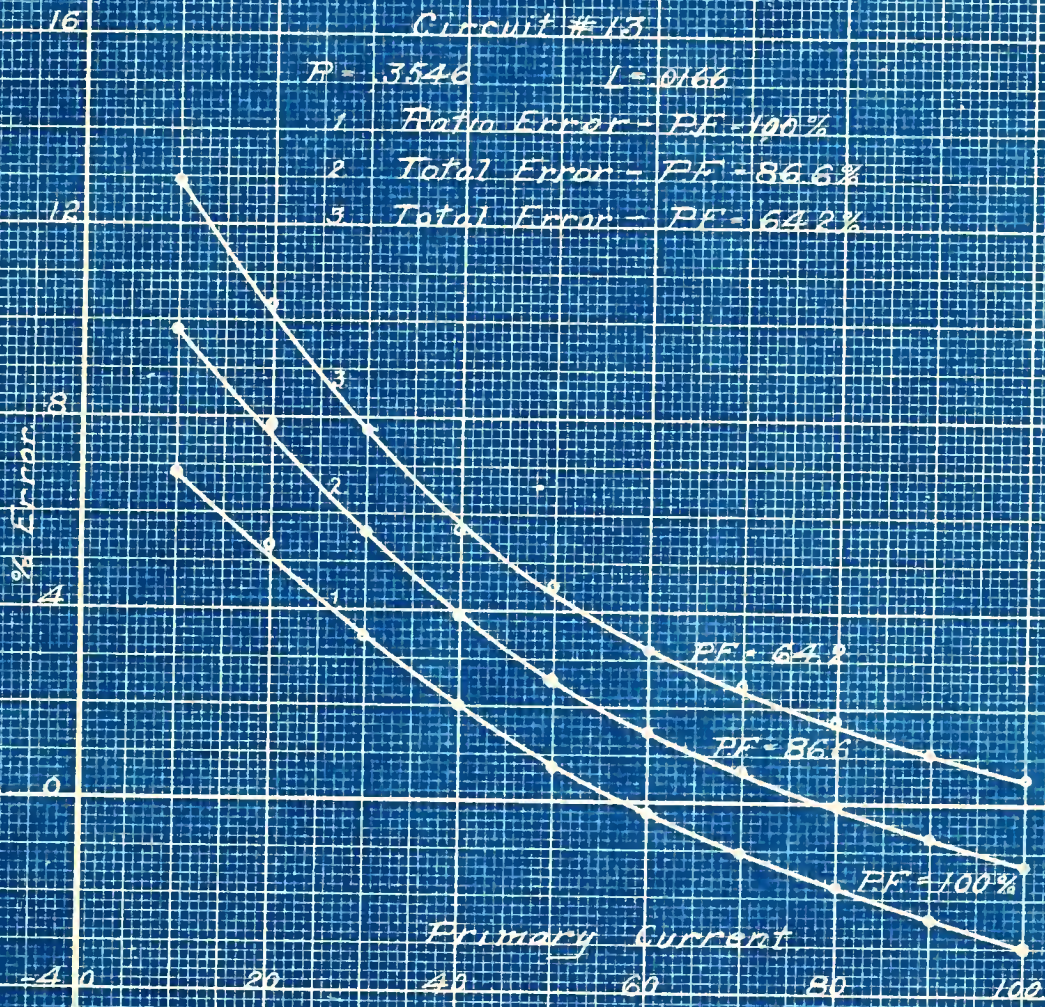

ARMOUR
INSTITUTE OF TECHNOLOGY
FUNDATION


Angle-Resistance Curves

For
25-50-75-100-125% Normal Load


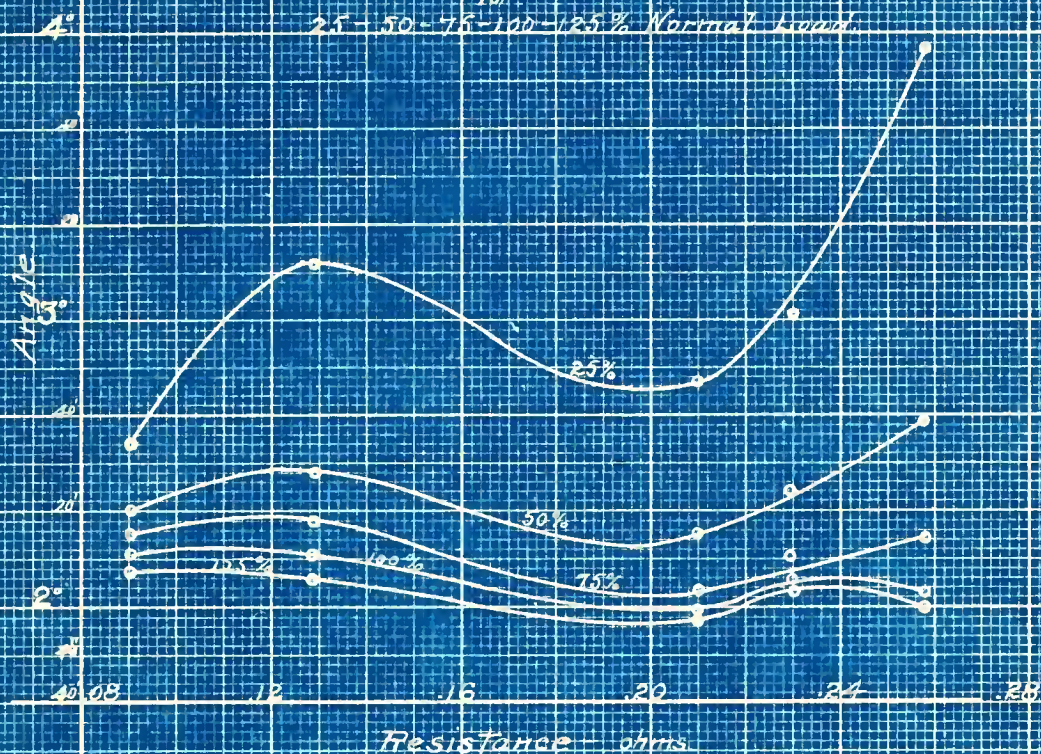


Ratio-Resistance Curves

For
25-50-75-100-125% Normal Load

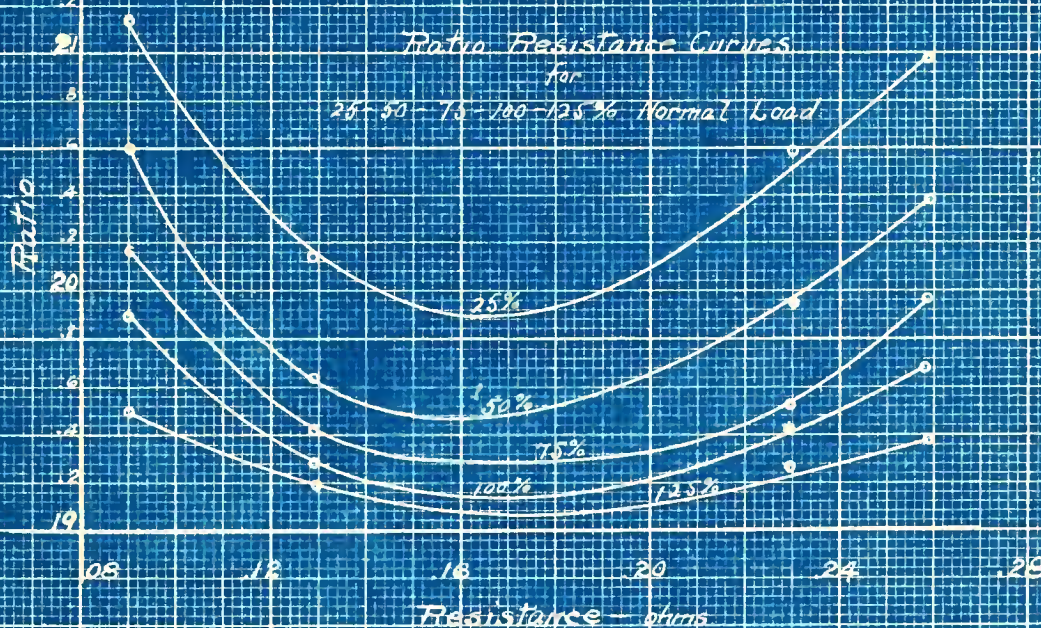


ARMOUR
INSTITUTE OF TECHNOLOGY
BOSTON,

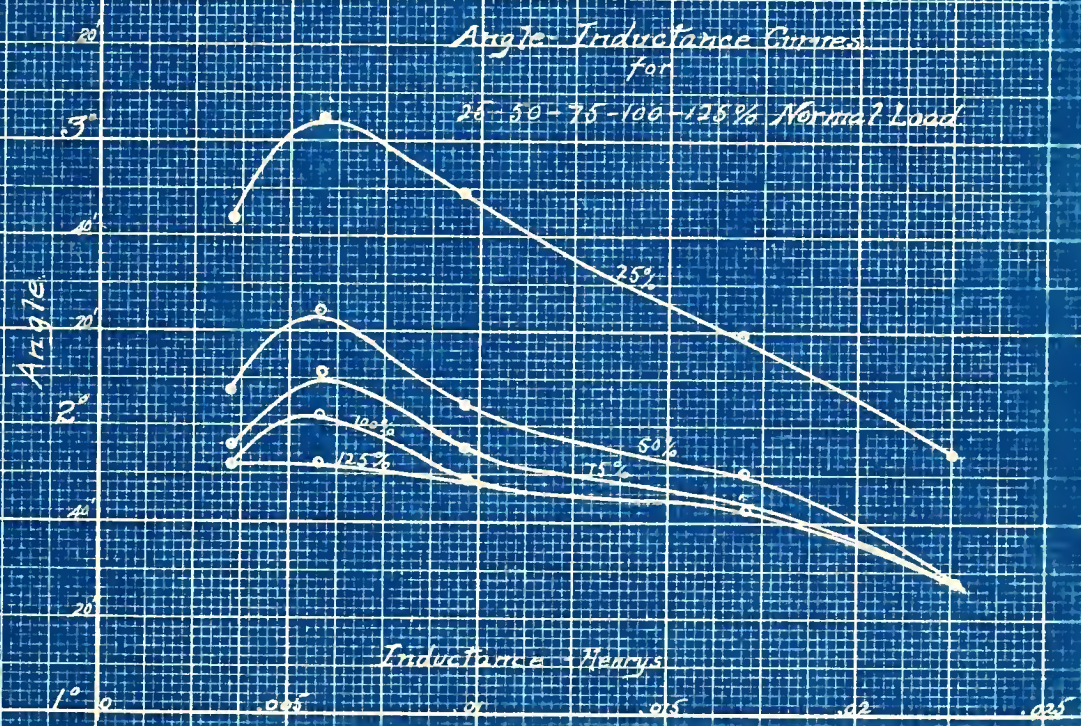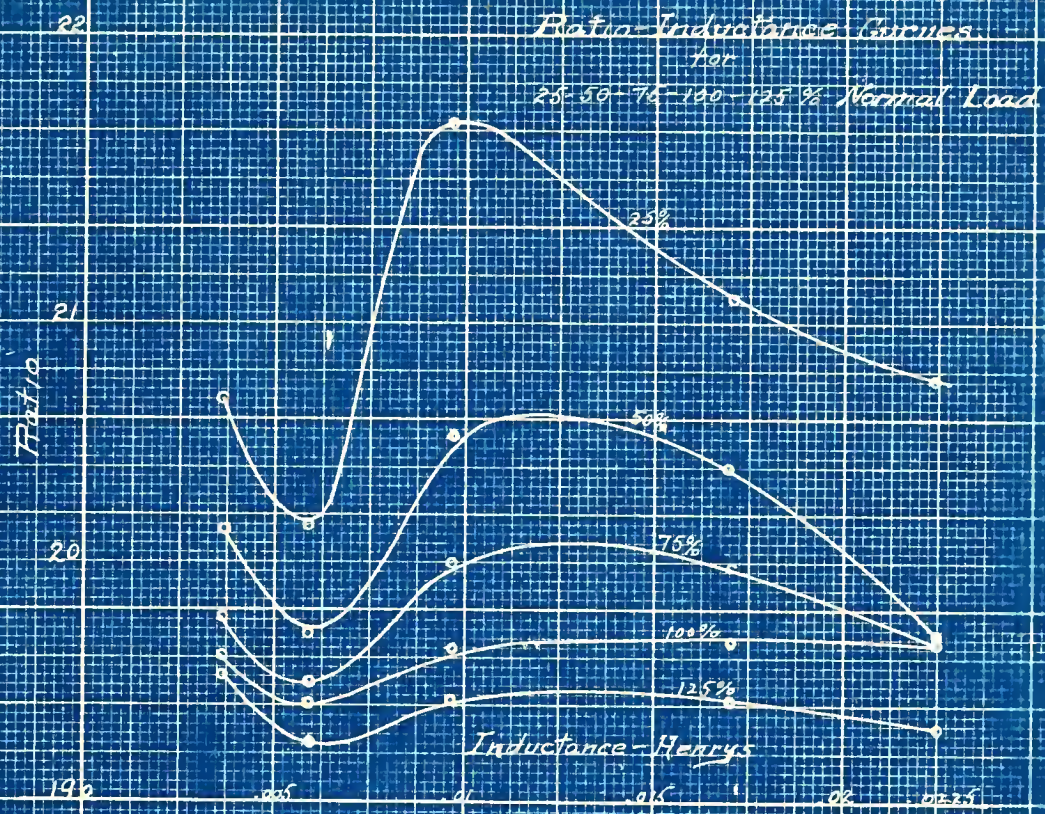


ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY,

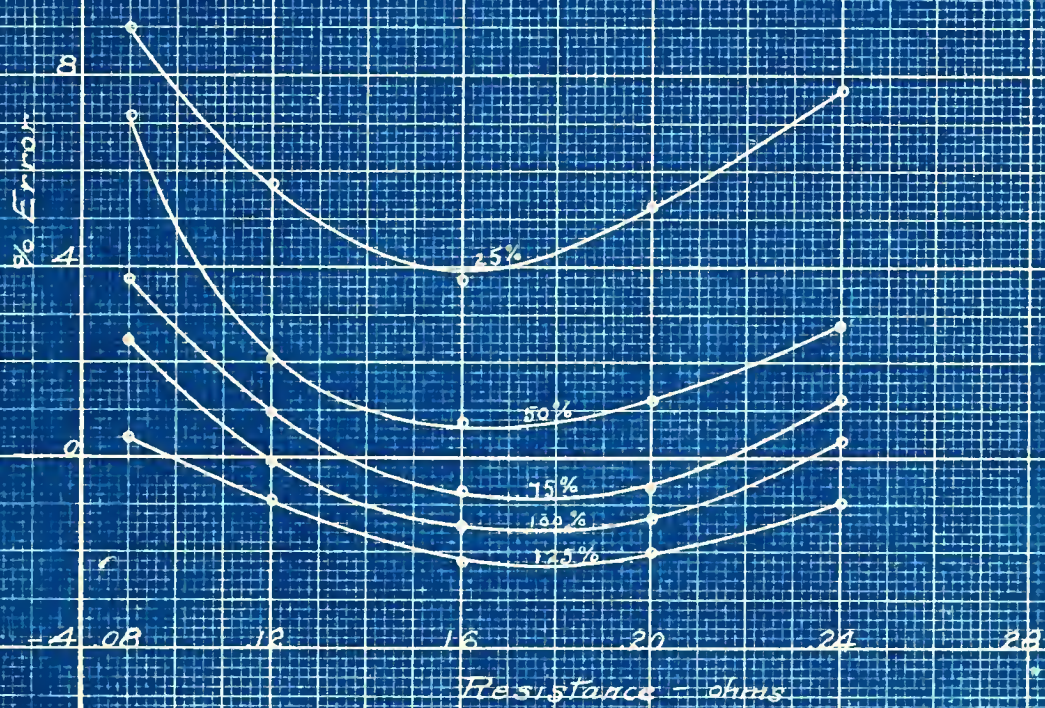Resistance-Error Curves
for
25 - 50 - 75 - 100 - 125 % Normal Load.




ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

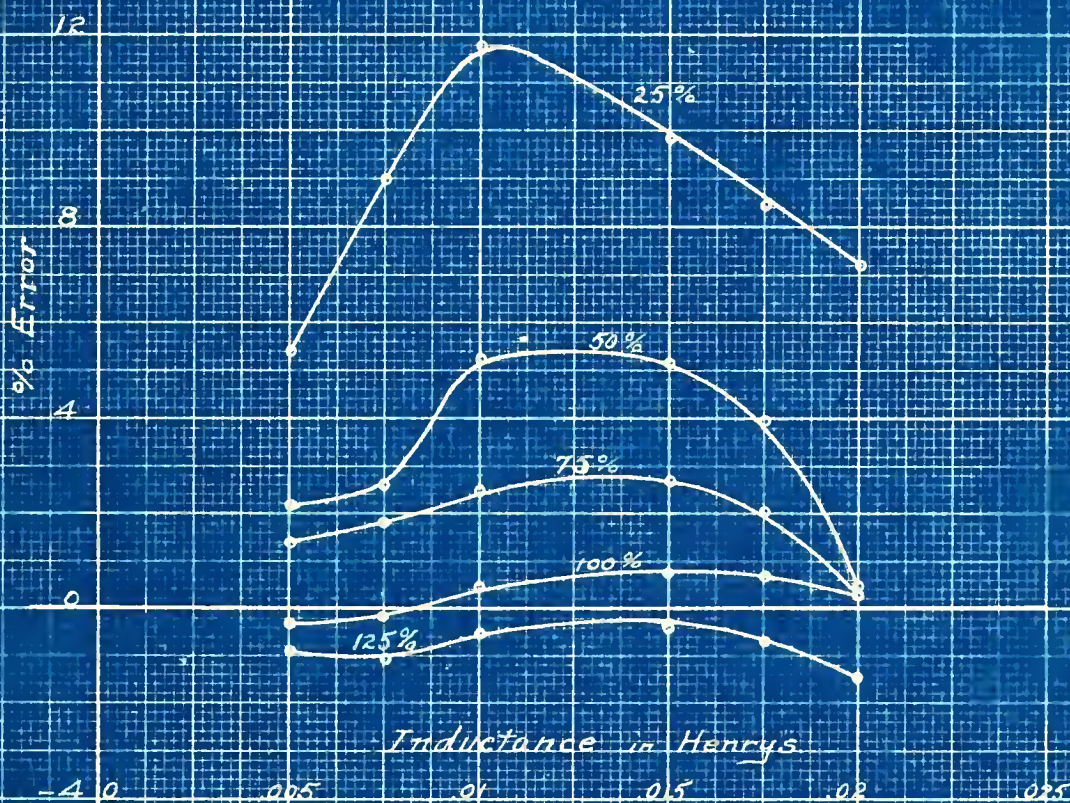Inductance - Error Curves
for
25 - 50 - 75 - 100 - 125 % Normal Load




ARMOUR
STATE OF TECHNOLOGY
1914

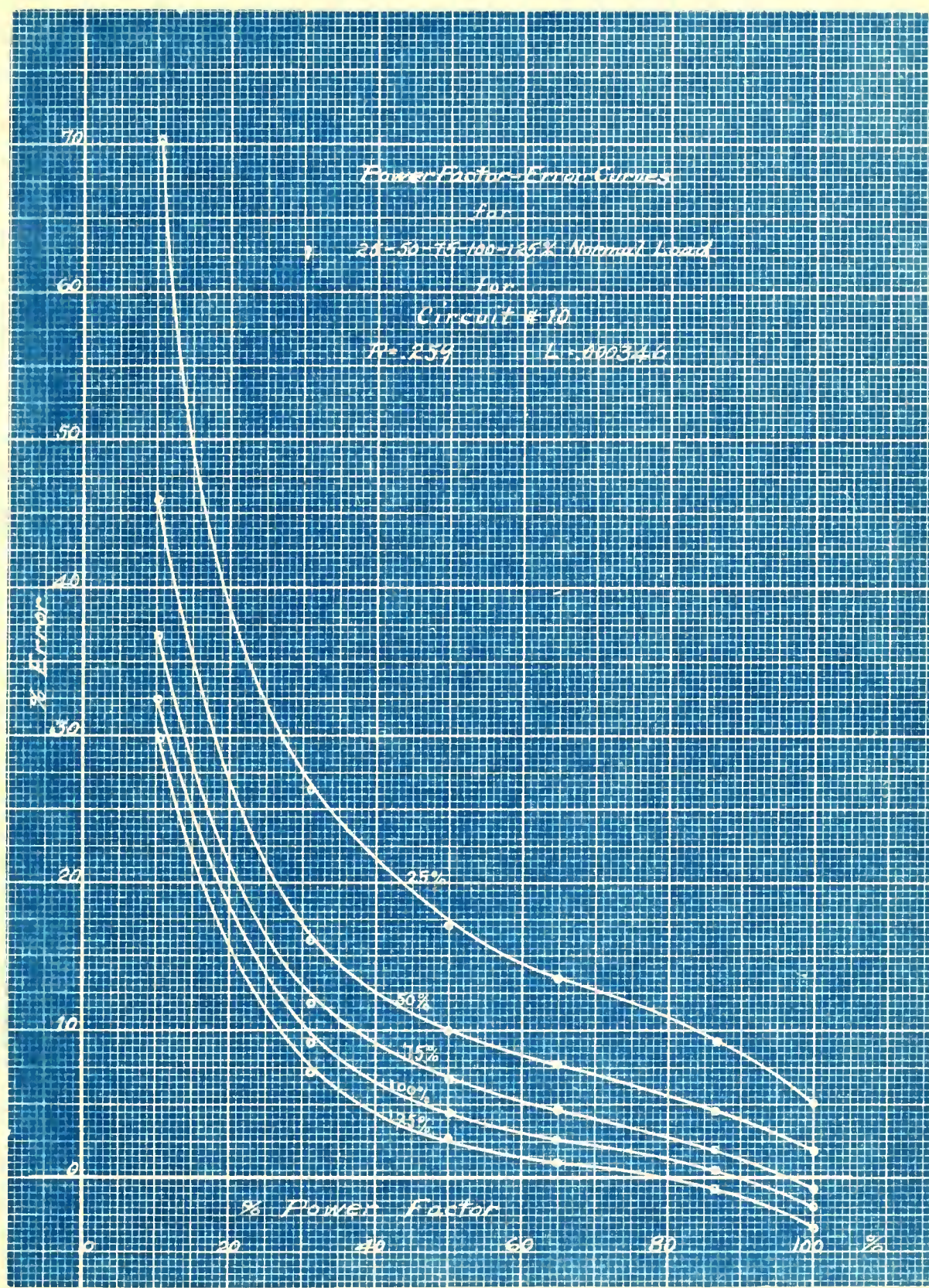


E.M.B.

V.F.V.

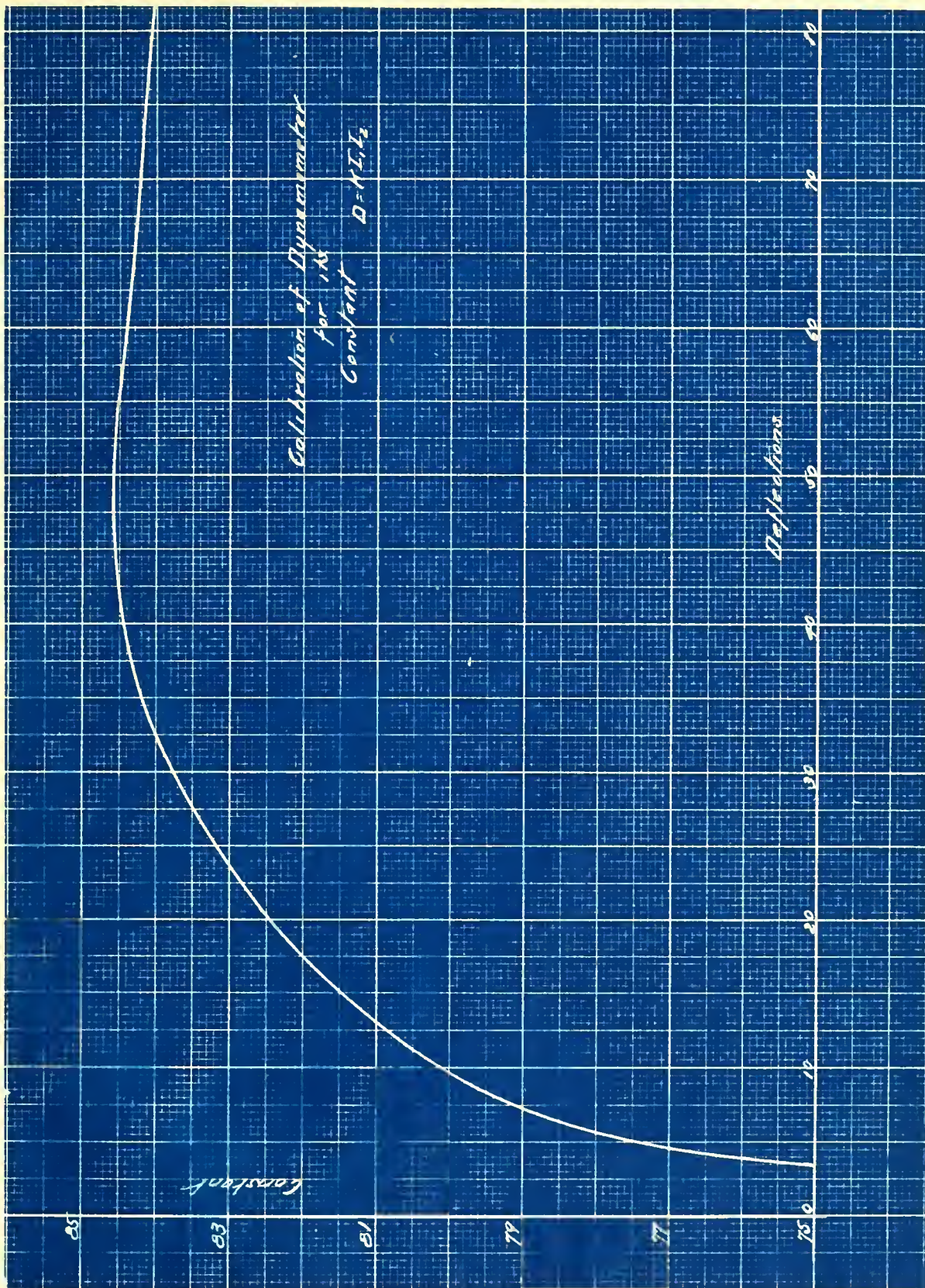
ARMOUR
INSTITUTE OF TECHNOLOGY
CHICAGO, ILL.



ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

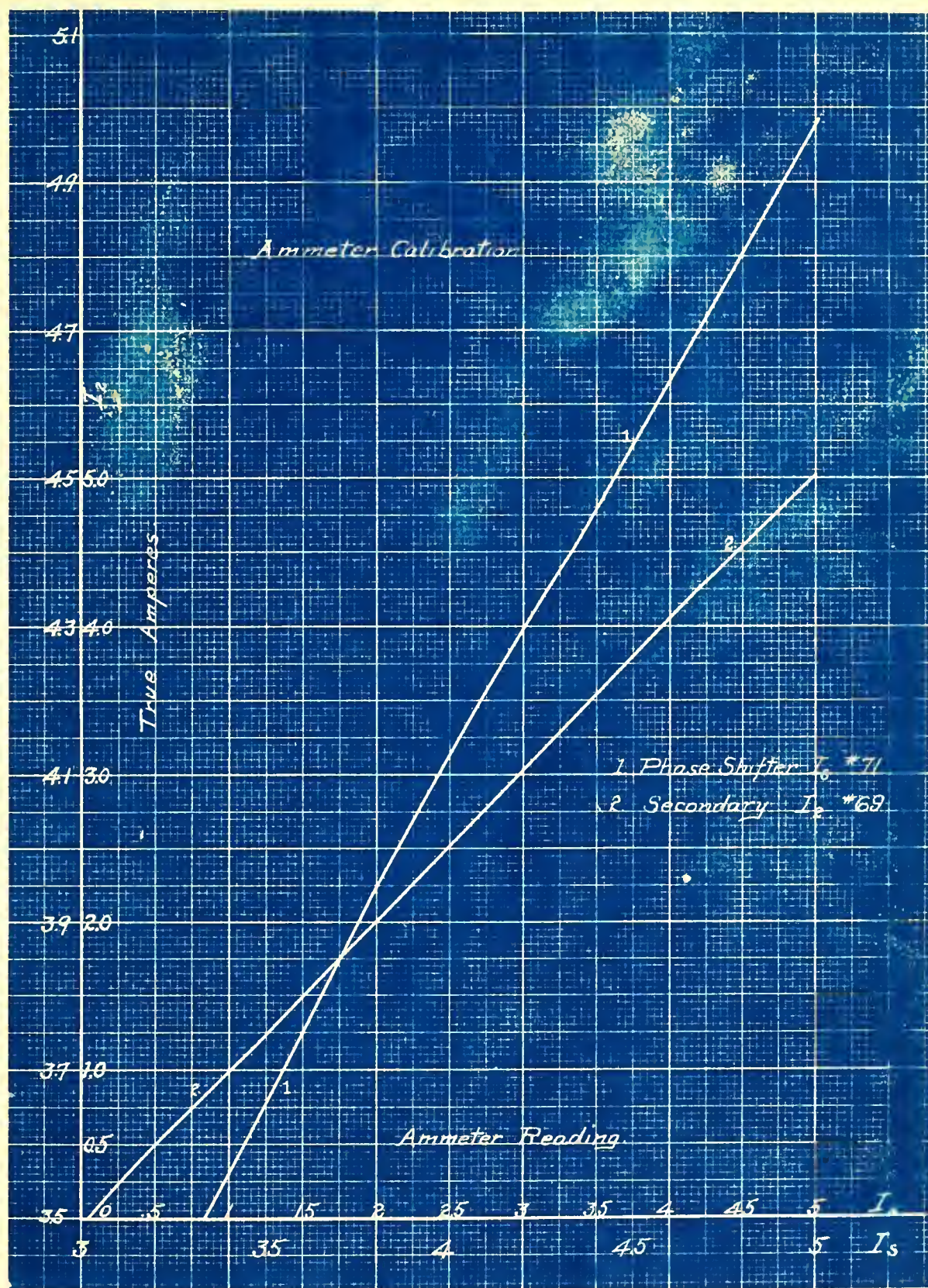

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY.

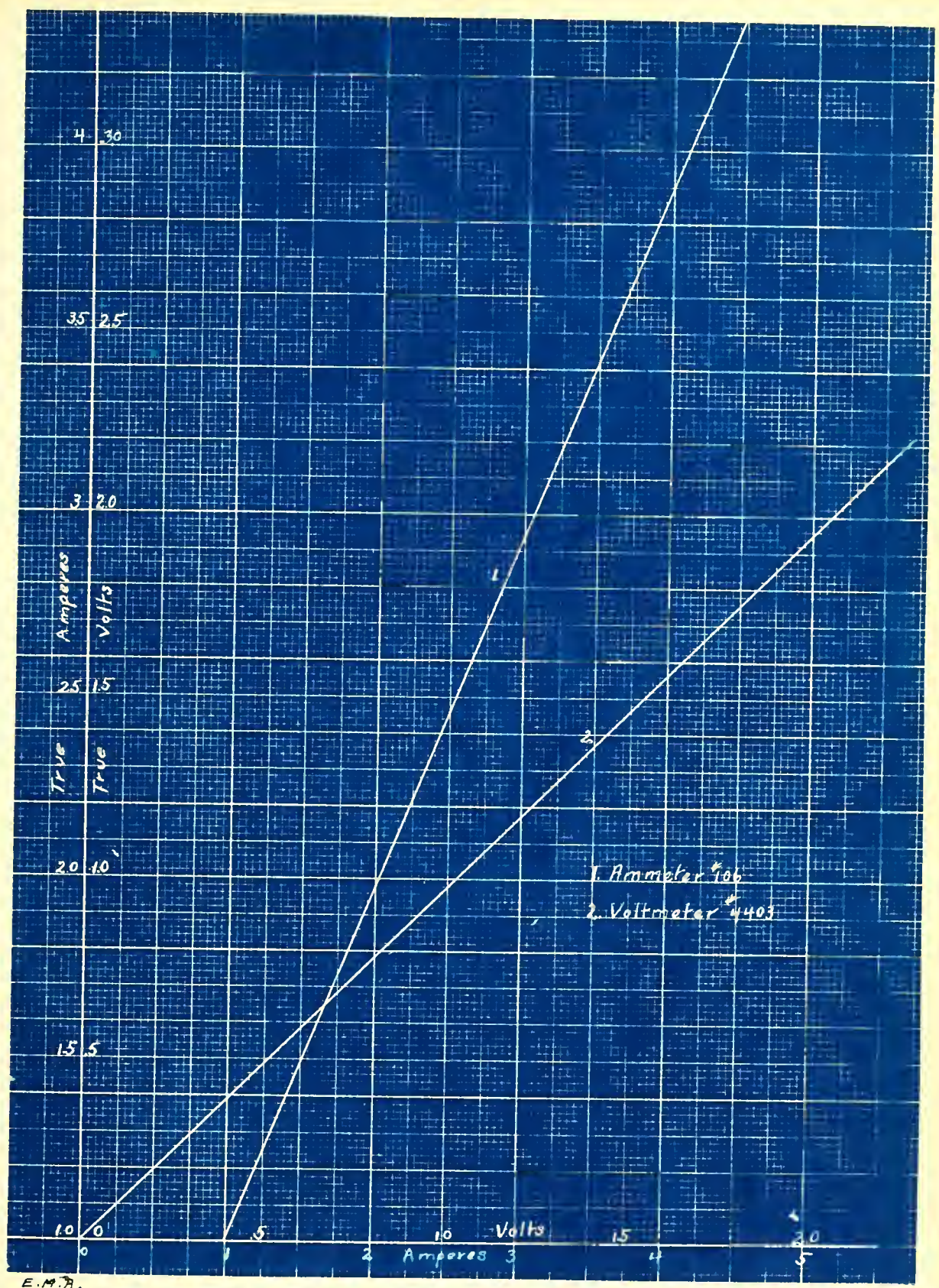

E.M.F.

V.F.V.

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY

Calibration Curves
of
Hot Wire Ammeter

Ampères
 I_0 50 40 30 20 10

25

20

15

10

5

0

Volts E_3

25

20

15

10

5

0

Volts E_3

25

20

15

10

5

0

Volts E_3

25

20

15

10

5

0

Volts E_3

ARMOUR
INSTITUTE OF TECHNOLOGY
LIBRARY



